

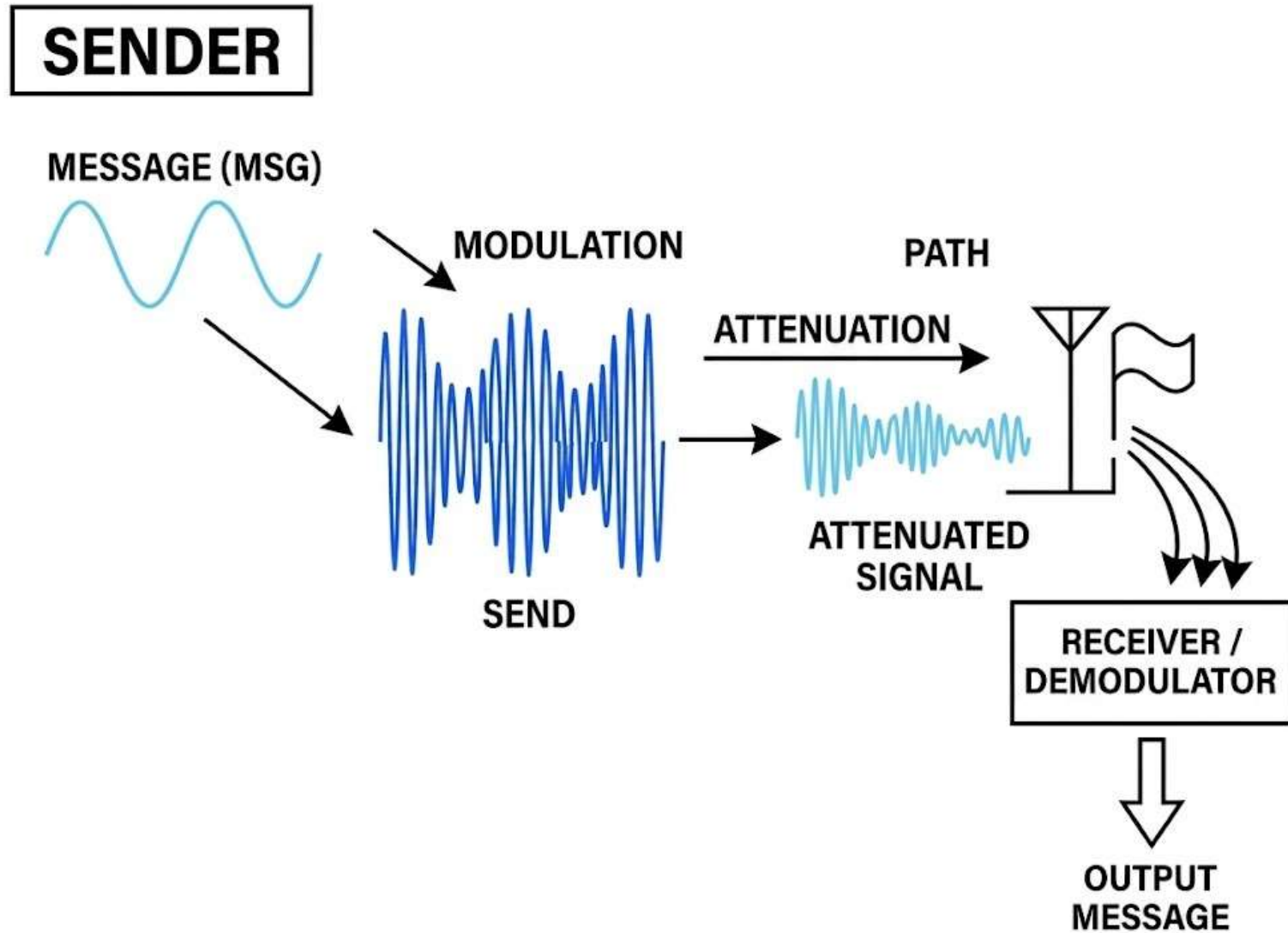


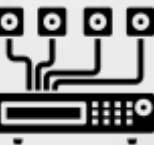

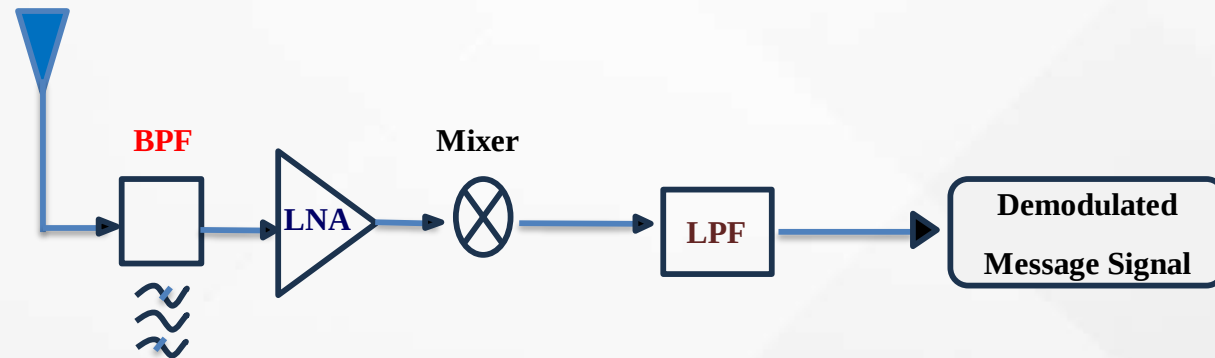Design of a 2.45 GHz RF Receiver in CMOS 45nm technology





Co-Supervisor:
Dr. Raqibul Mostafa
Professor, Dept. of EEE




Co-Supervisor:
Dr. Md. Hasanuzzaman
Associate Professor, Dept. of EEE




Chair:
Azad Hossain Saykat
021 221 017



Member:
Sazzad Hossen
021 221 026

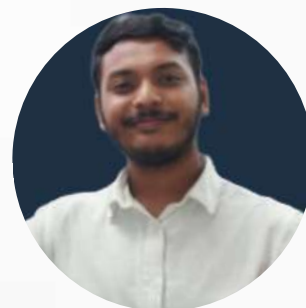

Recorder:
Suvom Karmakar
021 221 027

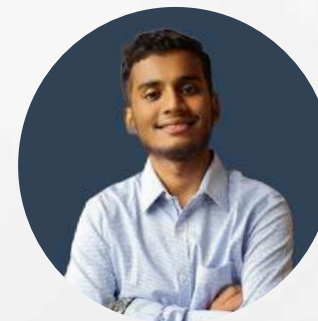

Member:
Md. Tahman Hossain
021 221 099

Table of Content



- Overview of RF Receiver
- Low Pass Filter
- Mixer
- Low Noise Amplifier
- Band Pass Filter
- Integrated RF Receiver
- Conclusion

Why RF Receivers Matter?



Motivation

- Compact and Low-power.
- RF front-end performance directly affects signal quality and power usage.
- Receiver performance defines signal sensitivity, power consumption, and noise tolerance.
- Global 2.45 GHz ISM Band.
- Single-Chip CMOS Integration.

Real-Life Applications

- Wireless communication: Wi-Fi, Bluetooth etc.
- Wearable devices



Block Diagram of RF Receiver Design



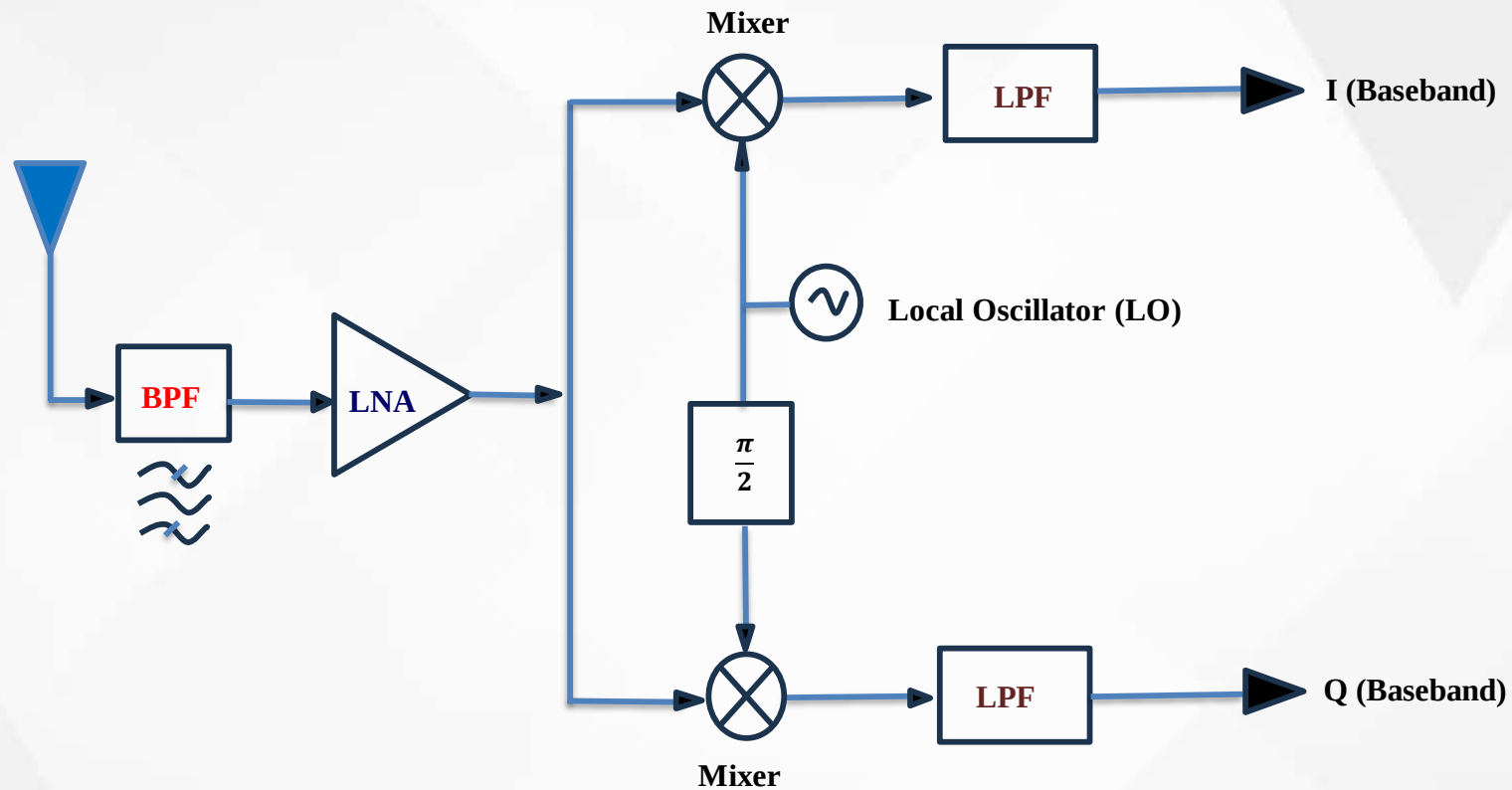
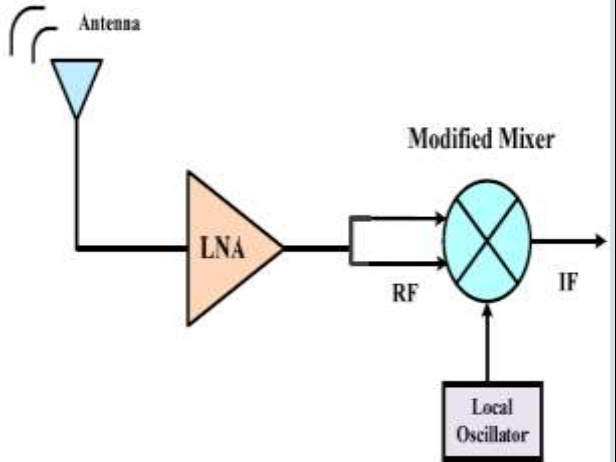


Figure: Proposed Block Diagram of the RF Receiver System

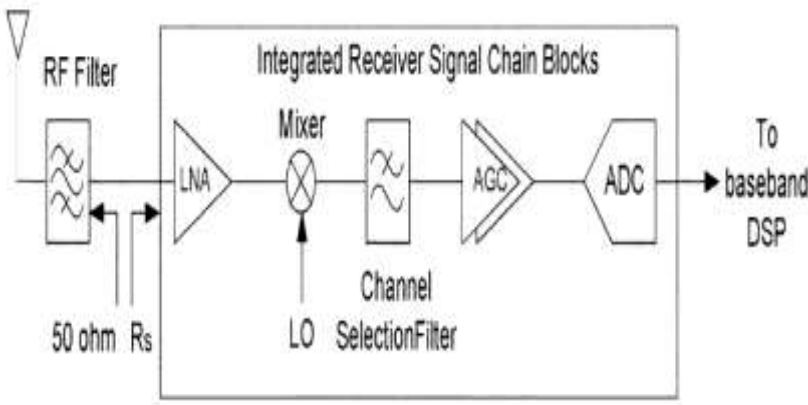

Literature Review

Paper Title	2.4 GHz Balunless Narrowband Receiver Front-End	CMOS RF Receiver System Design: A Systematic Approach	A Unified design Methodology for Front-end RF/mmWave Receivers
Block Diagram			
Reference	El-Desouki, M.M.; Qasim, S.M.; BenSaleh, M.S.; Deen, M.J. Toward Realization of 2.4 GHz Balunless Narrowband Receiver Front-End for Short Range Wireless Applications. <i>Sensors</i> 2015, 15, 10791-10805. https://doi.org/10.3390/s150510791	Wenjun Sheng, A. Emira and E. Sanchez-Sinencio, "CMOS RF receiver system design: a systematic approach," in <i>IEEE Transactions on Circuits and Systems I: Regular Papers</i>, vol. 53, no. 5, pp. 1023-1034, May 2006, doi: 10.1109/TCSI.2005.862286.	Michailidis, Anastasios, Alexandros Chatzis, Panayiota Tsimpou, Vasiliki Gogolou, and Thomas Noulis. 2025. "A Unified Design Methodology for Front-End RF/mmWave Receivers" <i>Electronics</i> 14, no. 2: 235. https://doi.org/10.3390/electronics14020235

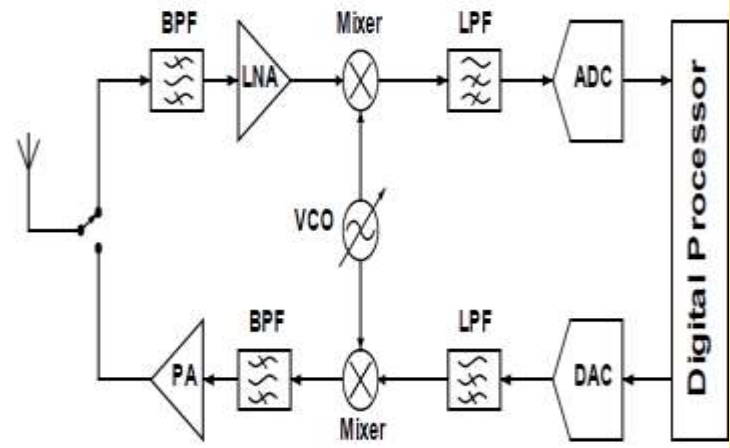

Proposed Improvements

1. 2.45 GHz LNA Optimization

Apply systematic S-parameter methodology for achieving 15-20 dB gain with < 3 dB noise figure at 1.2V supply.

2. CMOS Technology Scaling

Leverage 45nm CMOS advances for integrated system-level design to achieve target < 10 mW power consumption.

3. Integrated BPF Design

Implement optimized bandpass filtering for 2.45 GHz range with precise 20-100 MHz passband control.

4. System-Level Architecture

Focus on total RF receiver system integration for 2.45 GHz applications.



RF Receiver Block Specification

1

Low Noise Amplifier (LNA) Specification

Parameter	Value
Supply Voltage	1.2 V
Power Consumption	<2mW
NF (50 Ω)	< 3dB
Gain	15 - 20 dB
S11	$\leq$ -10dB
S22	$\leq$ -10dB
S21	15 – 20 dB
S12	$\leq$ -25dB

3

Band Pass Filter (BPF) Specification

Parameter	Value
Supply Voltage	1.2 V
Passband Width	20 MHz to 100 MHz
Center Frequency	2.45 GHz
Upper Cutoff Frequency	2.45 GHz + 10 MHz
Lower Cutoff Frequency	2.45 GHz - 10 MHz

2

Low Pass Filter (LPF) Specification

Parameter	Specification
Passband Frequency	20 MHz
Stopband Frequency	30 MHz
Stopband Attenuation	> 40 dB
Bandwidth	20 MHz
Passband Ripple	1dB
Source Impedance	50 ohm

4

Mixer Specification

Parameter	Specification
Supply voltage	1.2 V
Power Consumption	<2.5 mW
RF frequency	2.45 GHz
Lo Frequency	2.43GHz
Conversion Gain	>10 dB



Passive Low Pass Filter

Theoretical Background



Chebyshev low-pass element values (1-rad/s bandwidth)									
n	L_1	C_2	L_3	C_4	L_5	C_6	L_7	C_8	R_2
1.0-dB ripple									
3	2.0236	0.9941	2.0236						1.0000
5	2.1349	1.0911	3.0009	1.0911	2.1349				1.0000
7	2.1666	1.1115	3.0936	1.1735	3.0936	1.1115	2.1666		1.0000

Table: Coefficients of the Chebyshev lowpass prototype filter normalized to 1 rad/s corner frequency and 1Ω impedance.

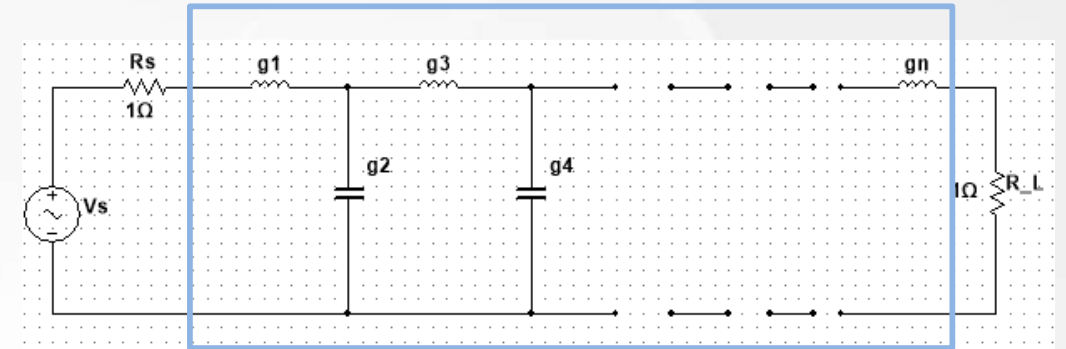


Fig. Nth Order Passive Low Pass Filter Prototype

Equations for Conversion of Normalize Value into Actual Circuit Element

Series Inductors:
$$L_k = \frac{R_s * g_k}{w_c}$$

Shunt Capacitors:
$$C_k = \frac{g_k}{R_s * w_c}$$



Passive Low Pass Filter

Calculation

Component	Type	Index (n)	Formula	Value	Units
Rs	Source Impedance	g0		50	Ω
L1	Series Inductor	g1 = 2.1666	$L1 = R_s \cdot g1 / \omega_c$	862.08	nH
C2	Shunt Capacitor	g2 = 1.1115	$C2 = g2 / R_s \cdot \omega_c$	176.9	pF
L3	Series Inductor	g3 = 3.0936	$L3 = R_s \cdot g3 / \omega_c$	1230.96	nH
C4	Shunt Capacitor	g4 = 1.1735	$C4 = g4 / R_s \cdot \omega_c$	186.77	pF
L5	Series Inductor	g5 = 3.0936	$L5 = R_s \cdot g5 / \omega_c$	1230.96	nH
C6	Shunt Capacitor	g6 = 1.1115	$C6 = g6 / R_s \cdot \omega_c$	176.9	pF
L7	Series Inductor	g7 = 2.1666	$L7 = R_s \cdot g7 / \omega_c$	862.08	nH
RL	Load Impedance	g8		50	Ω

Low Pass Filter (LPF) Specification

Parameter	Specification
Passband Frequency	20 MHz
Stopband Frequency	30 MHz
Stopband Attenuation	> 40 dB
Bandwidth	20 MHz
Passband Ripple	1dB
Source Impedance	50 ohm
Load Impedance	50 ohm


Chebyshev Type I:

$$N = \frac{\cosh^{-1} \left(\frac{\sqrt{10^{\left(\frac{A_s}{10}\right)} - 1}}{\sqrt{10^{\frac{A_p}{10}} - 1}} \right)}{\cosh^{-1} \left(\frac{f_s}{f_p} \right)} = 7^{th} \text{ (Order)}$$




Passive Low Pass Filter

Schematic Diagram

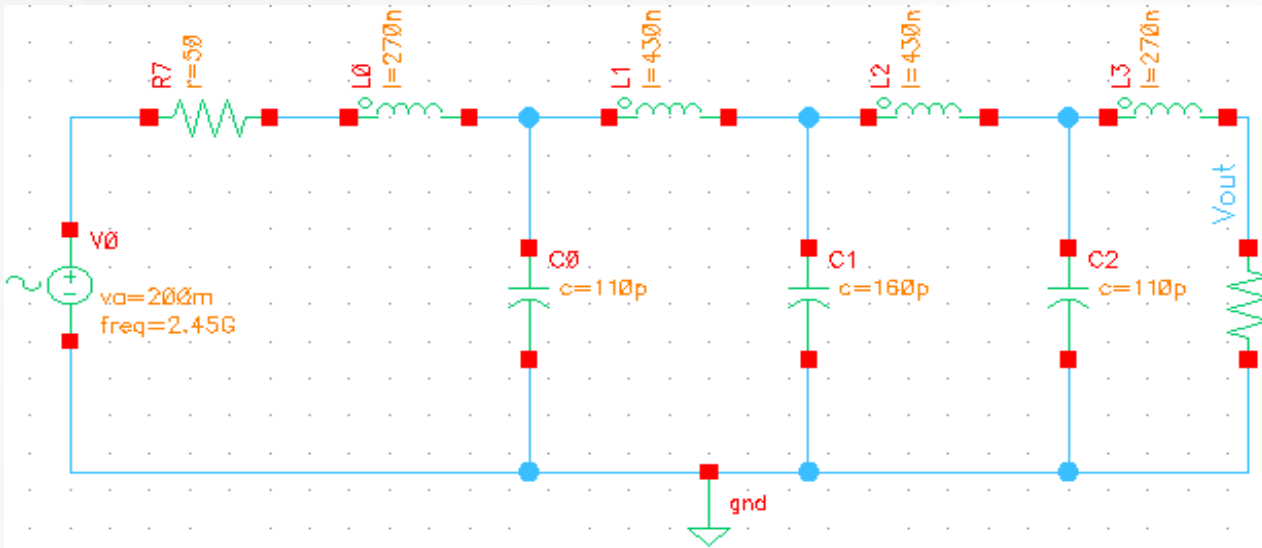

AC Analysis

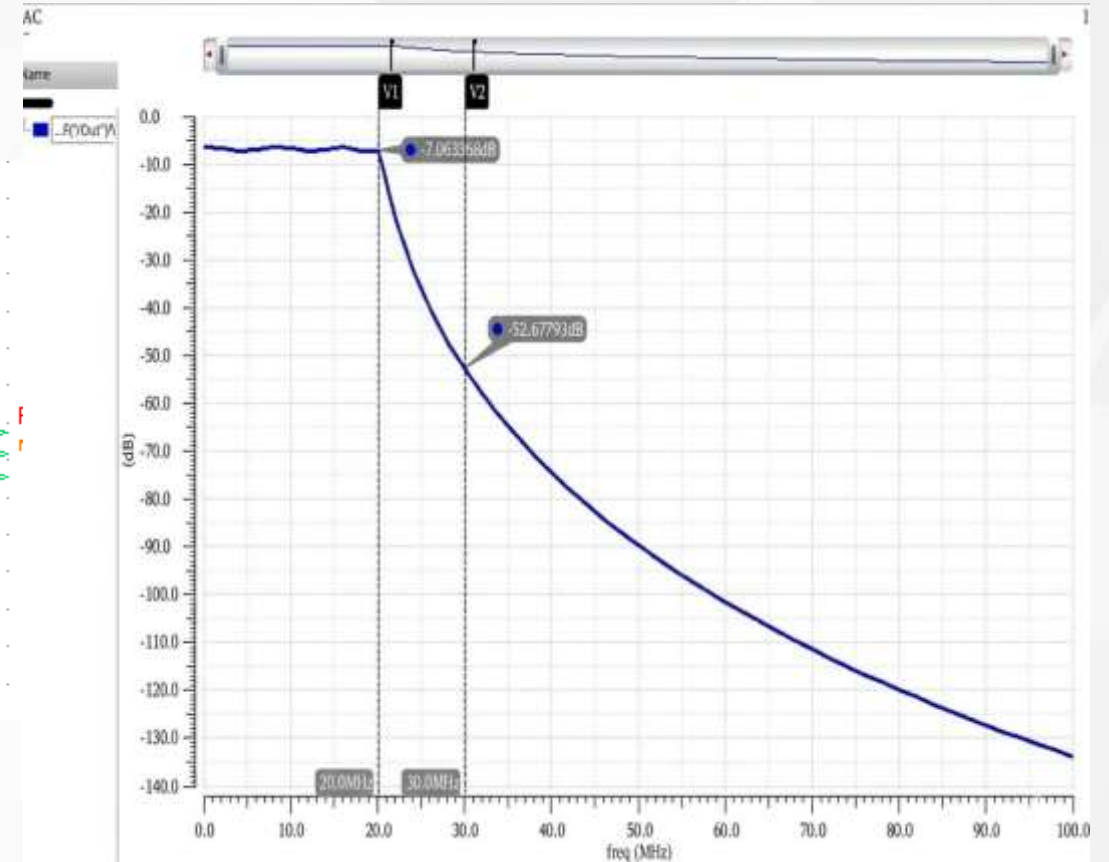

Active Low Pass Filter

Block Diagram

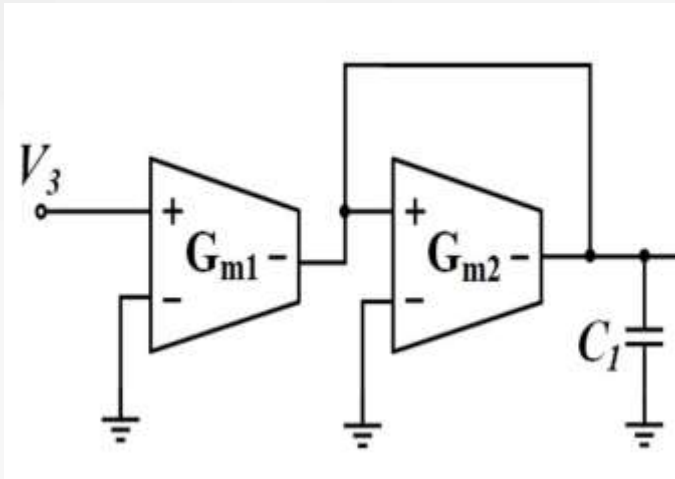



Fig. 1st Order Gm-C Filter Block Diagram



Power Consumption

$$= 124\mu A * 1.2V = 0.15mW$$

Schematic Diagram

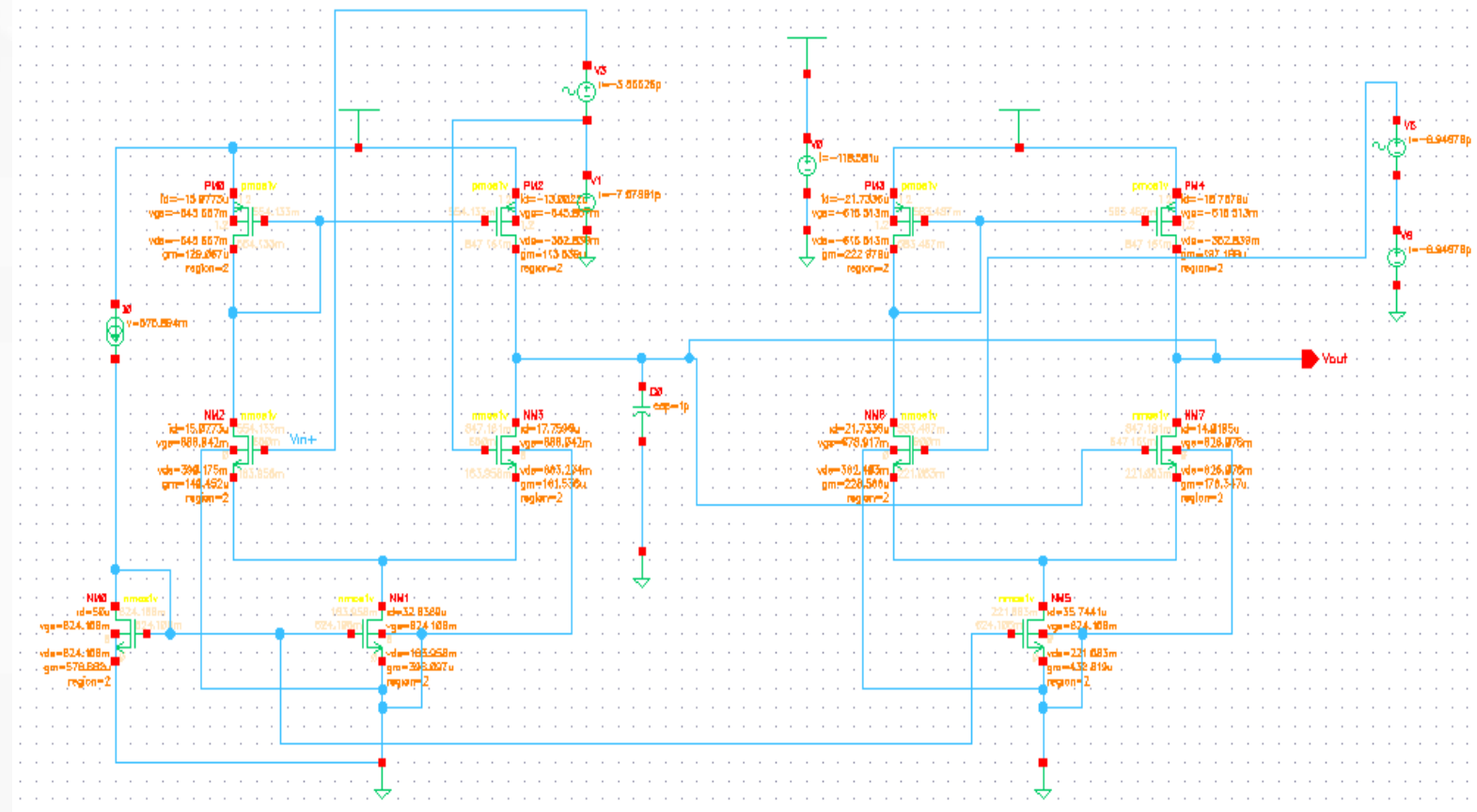


Azad Hossain Saykat
021 221 017




Active Low Pass Filter

Transient Analysis

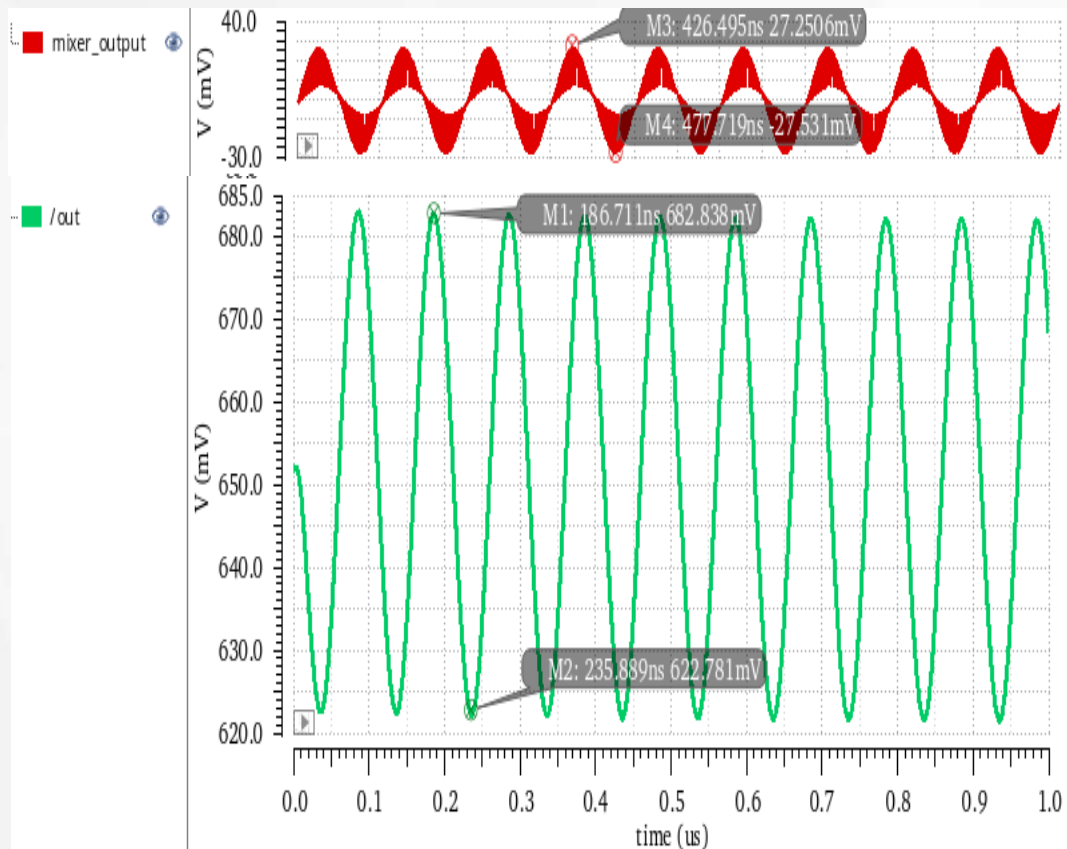


AC Analysis

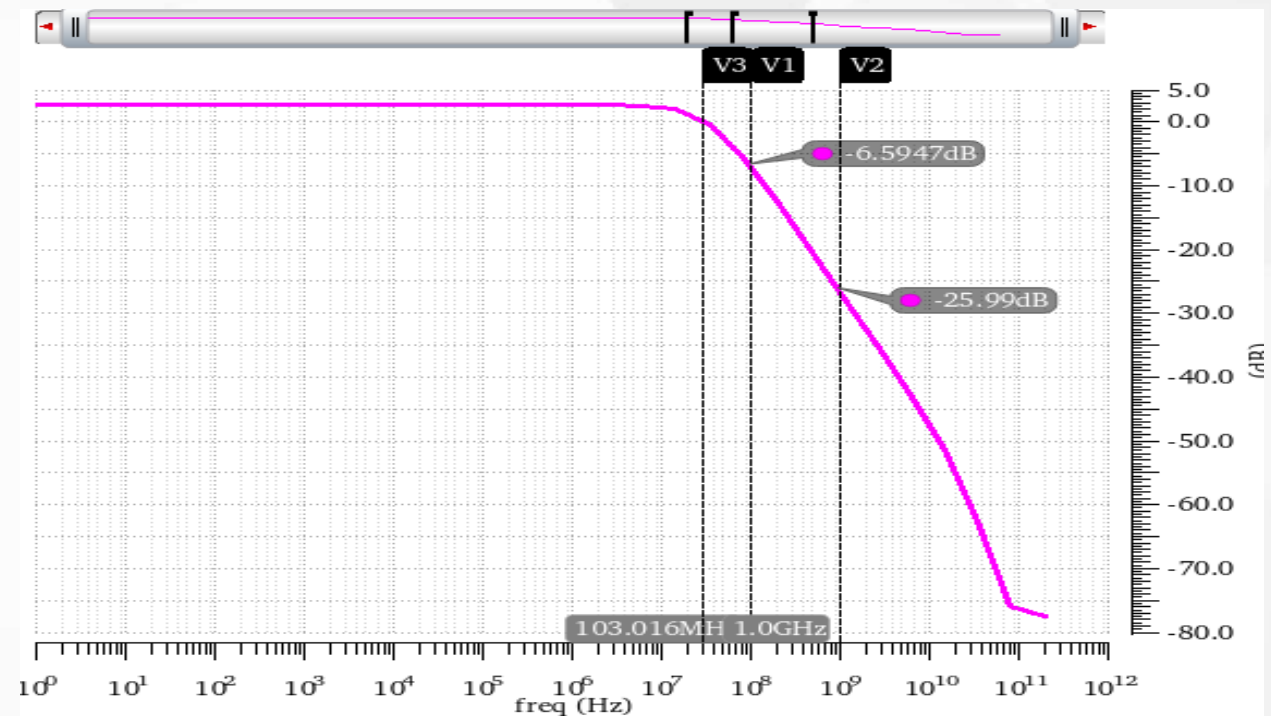


Active 2nd Order Low Pass Filter


Block Diagram

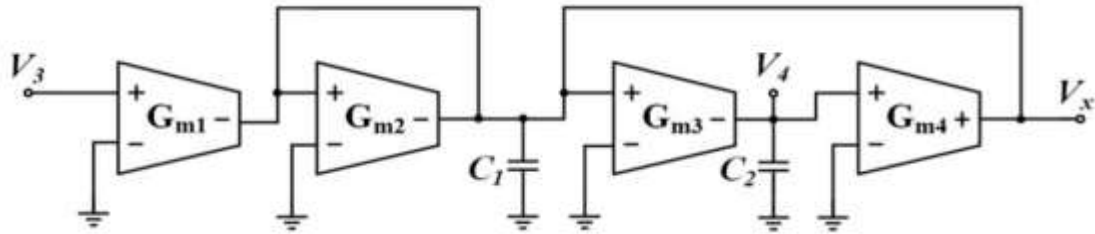

Circuit Diagram

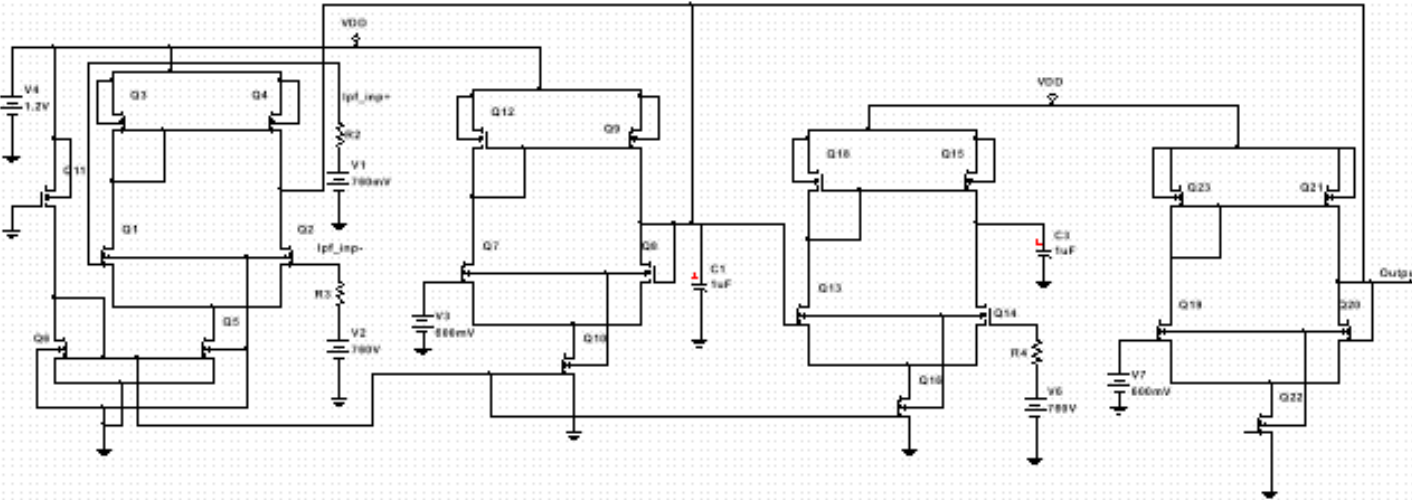

AC Analysis

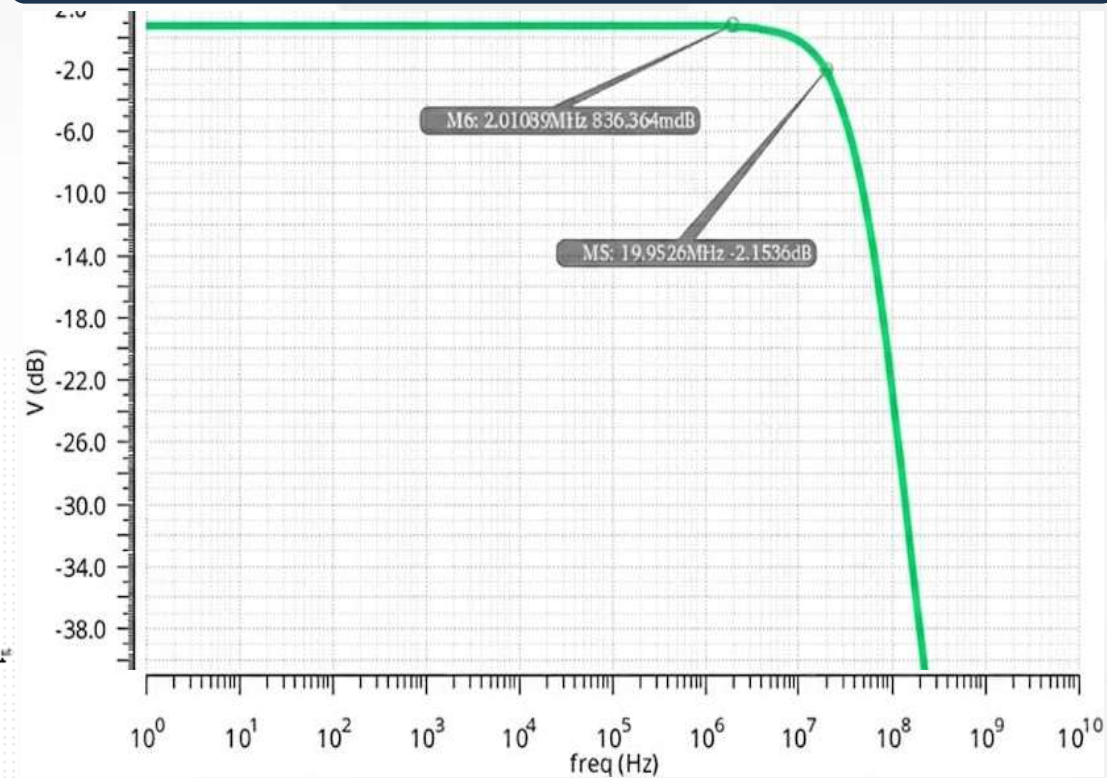

Power Consumption
= $182\mu A * 1.2V = 0.22mW$





Azad Hossain Saykat
021 221 017



Mixer

Theoretical Background

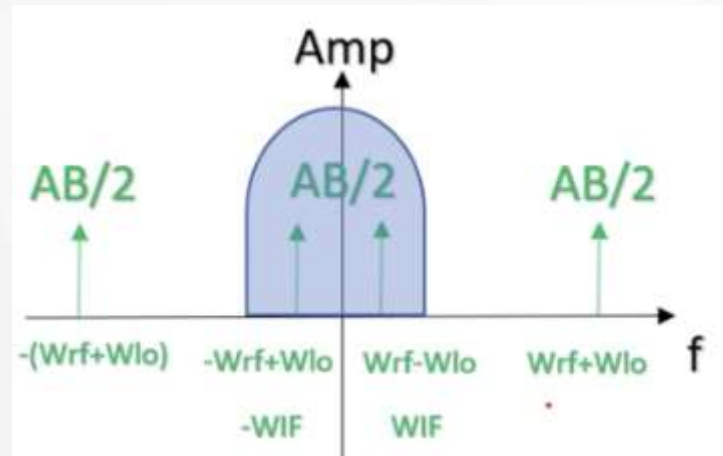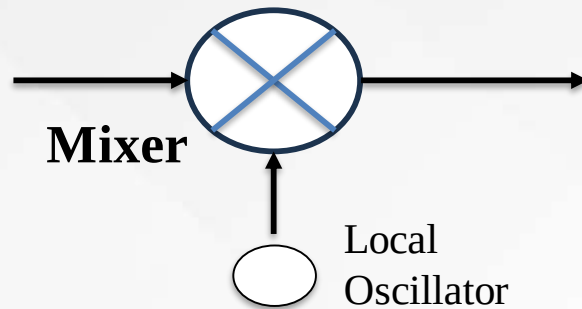

Mixer

To convert a high-frequency RF signal (2.45 GHz) down to a lower IF signal for easier filtering or processing.


It does this by multiplying the RF signal with a Local Oscillator (LO) signal:

$$v_{IF}(t) = v_{RF}(t) \times v_{LO}(t)$$

Because of trigonometric properties:

$$\cos(\omega_{RF}t)\cos(\omega_{LO}t) = \frac{1}{2}[\cos(\omega_{RF} - \omega_{LO})t + \cos(\omega_{RF} + \omega_{LO})t]$$

output contains sum and difference frequencies (IF = |RF – LO|).


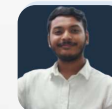


Suvom Karmakar
021 221 027



Mixer

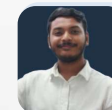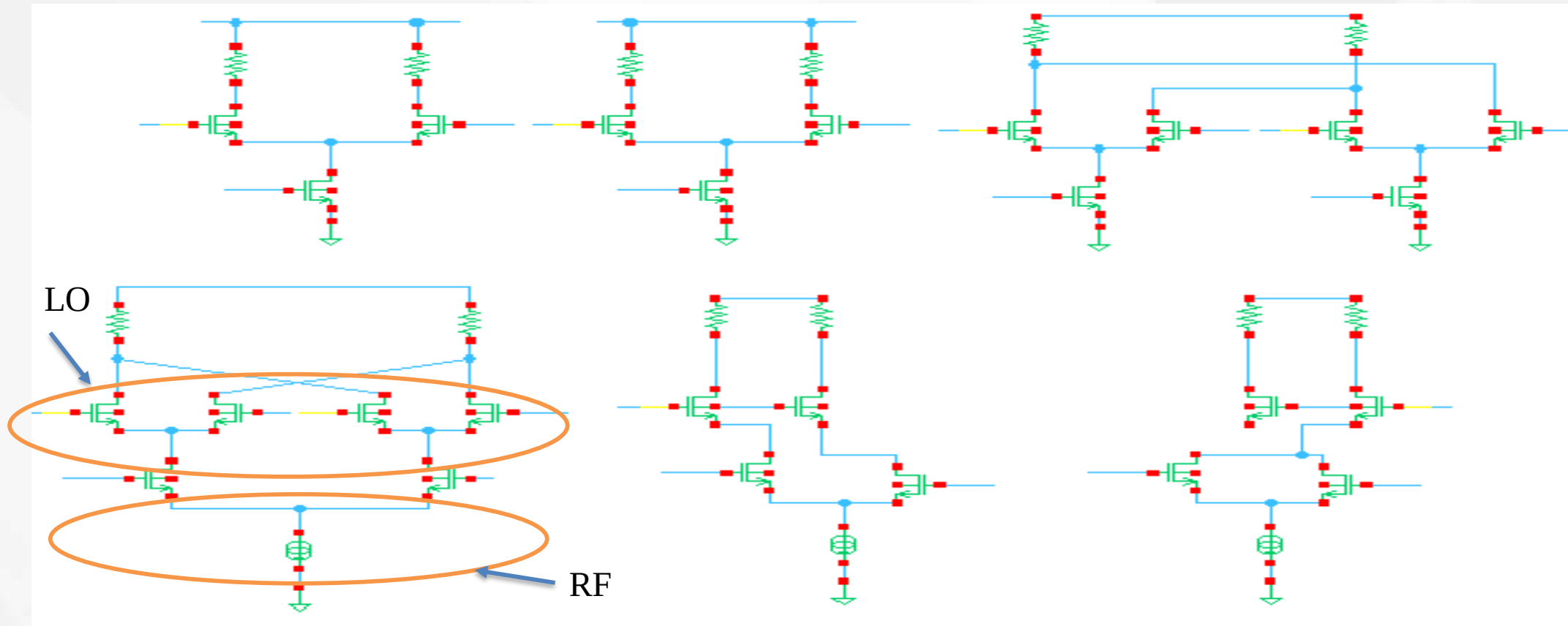How the Gilbert Cell Circuit is Developed?



Suvom Karmakar
021 221 027




Mixer

Calculation


Parameter	Specification
Supply voltage	1.2 V
Power Consumption	<2.5 mW
RF frequency	2.45 GHz
Lo Frequency	2.43Ghz
Conversion Gain	>10 dB
Load Resistance	1k ohm
B_{eff}	$\frac{362\mu A}{V^2}$
V_{th}	355mV

Type	Formula	Value	Units
Bias Current	$I_{bias} = \frac{P}{2}$	1.25	mA
Current per Branch	$I_d = \frac{I_{bias}}{2}$	0.625	mA
Transconductance	$g_m = \frac{(A_v * \pi)}{2 * R_{load}}$	15.708	mS
Rf Overdrive Voltage	$V_{ov} = 2 * \frac{I_d}{g_m}$	80	mV
RF Stage (M1, M2) Sizing	$\frac{W}{L} = \frac{2 * I_d}{B_{eff} * V_{ov}^2}$	528.6	-
LO Source Voltage	$V_{S_{Lo}} = V_{cm_{rf}} - V_{th}$	0.405	V
LO Overdrive Voltage	$V_{ov} = V_{cm_{lo}} - V_{S_{Lo}} - V_{th}$	0.1	V
LO Stage Sizing	$\frac{W}{L} = \frac{2 * I_d}{B_{eff} * V_{ov}^2}$	345.3	-
Tail Sizing	$\frac{W}{L} = \frac{2 * I_d}{B_{eff} * V_{ov}^2}$	83.6	-

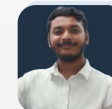

Mixer

Schematic Diagram

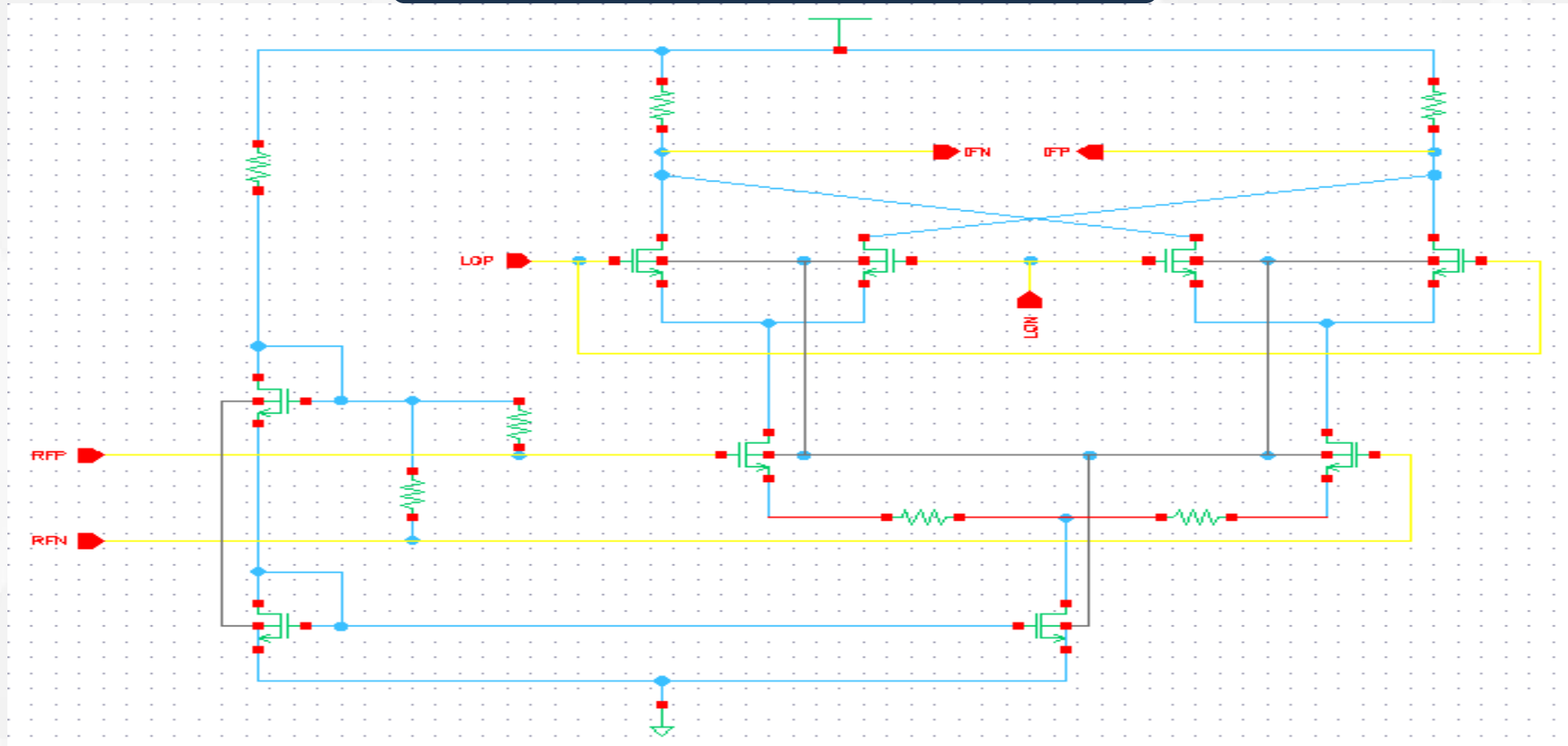

Power Consumption = $2.51mW$




Suvom Karmakar
021 221 027




Mixer

Transient Analysis

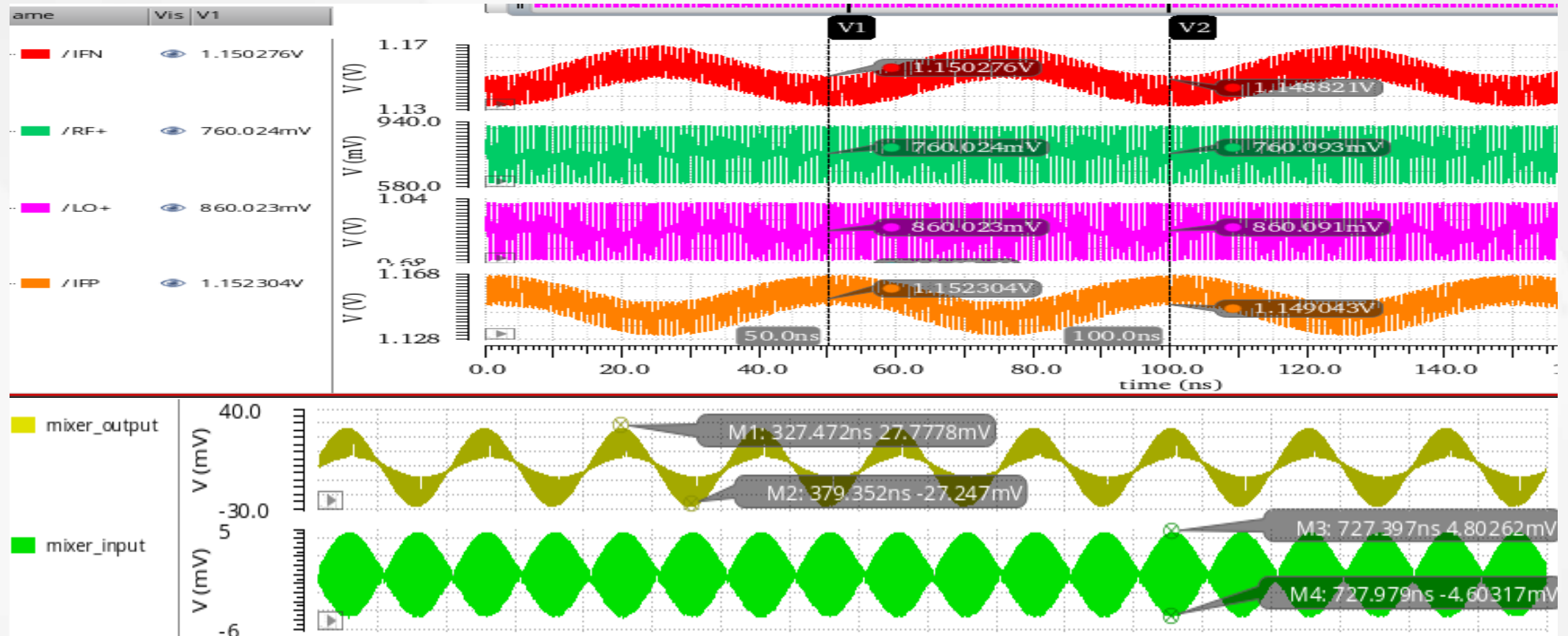

Gain = 15.34 dB

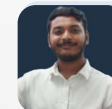

Suvom Karmakar
021 221 027




Low Noise Amplifier

Description



- ❑ The LNA amplifies the weak received signal with minimal noise.

Low Noise Amplifier (LNA) Specification	
Parameter	Value
Supply voltage	1.2 V
Power Consumption	2mW
Frequency	2.45 GHz
NF (50 Ω)	< 3dB
Gain	15 - 20 dB
S11(Input Return Loss)	≤ -10 dB
S22(Output Return Loss)	≤ -10 dB
S21(Forward Gain)	15dB - 20dB
S12(Reverse Isolation)	≤ -25 dB

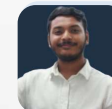

Low Noise Amplifier

Theoretical Background


$$\text{Input impedance, } Z_{in} = R_g + R_{Ls} + R_{Lg} + s(L_s + L_g) + \frac{1}{sC_{gst}} + \frac{g_m}{C_{gst}} L_s$$

$$R_e(Z_{in}) = \frac{g_m}{C_{gst}} L_s = w_t L_s = R_s$$

$$\text{Im}(Z_{in}) = w(L_s + L_g) - \frac{1}{w C_{gst}} = 0$$

Some transistor parameters in 45 nm technology are,


Parameter	Value
Supply Voltage	VDD = 1.2 V
Transistor Length	L = 180 nm (Minimum length: 45 nm, set to 4 times minimum)
Threshold Voltage	$V_{th} = 0.32 \text{ V}$
Electron Mobility	$\mu = 220 \frac{\text{cm}^2}{\text{v.s}}$
Gate Oxide Thickness	$t_{ox} = 1.8 \text{ nm}$

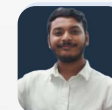

Low Noise Amplifier


Calculation

Step	Calculation Details	
(I)	$I_D = \frac{P_D}{V_{DD}} = \frac{2 \text{ mW}}{1.2 \text{ V}} = 1.667 \text{ mA}$	(IX) $\text{Gain} = g_m R_p = 10 \Rightarrow R_p = \frac{10}{g_m} = \frac{10}{31.25 \text{ mA/V}} = 320 \Omega$
(II)	$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.9 \times 8.854 \times 10^{-12}}{1.8 \text{ nm}} = 19.183 \times 10^{-3} \text{ mF/m}^2$	(X) $Q = \sqrt{\frac{R_p}{R_e} - 1} = \sqrt{\frac{320}{50} - 1} = 2.32$
(III)	$W_{opt} = \frac{1}{3W_0 L C_{ox} R_d} = \frac{1}{3 \times (2\pi \times 2.45 \times 10^9 \times 180 \times 10^{-9} \times 19.183 \times 10^{-3} \times 50)} = 125 \mu\text{m}$	(XI) $Q = \frac{R_p}{\omega_0 L_d} = L_d = \frac{320}{2\pi \times 2.45 \times 10^9 \times 2.32} = 8.94 \times 10^{-9} \text{ H}$
(IV)	$g_m = \sqrt{2\mu_n C_{ox} \frac{W_{opt}}{L} I_D} = \sqrt{2 \times 22 \times 10^{-3} \times 19.183 \times 10^{-3} \times \frac{125 \times 10^{-6}}{180 \times 10^{-9}} \times 1.667 \times 10^{-3}} = 31.25 \text{ mA/V}$	(XII) $C_d = \frac{1}{\omega_0^2 L_d} = \frac{1}{(2\pi \times 2.45 \times 10^9)^2 \times 8.94 \times 10^{-9}} = 471.81 \text{ fF}$
(V)	$C_{gst} = \frac{g_m L_d}{R_e} = \frac{31.25 \times 10^{-3} \times 2 \times 10^{-9}}{50} = 1.25 \text{ pF}$	(XIII) $V_{gs} = V_{th} + \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} = 0.32 + \sqrt{\frac{2 \times 1.667 \times 10^{-3}}{22 \times 10^{-18} \times 19.183 \times 10^{-3} \times 125 \times 10^{-6}}} = 420 \text{ mV} \approx 500 \text{ mV}$
(VI)	$C_{gs \text{ mos}} = \frac{2}{3} W_{opt} L C_{ox} = \frac{2}{3} \times 125 \times 10^{-6} \times 180 \times 10^{-9} \times 19.18 \times 10^{-3} = 287.75 \text{ fF}$	(XIV) $L_m = \frac{Q \times 50}{\omega_0} = \frac{2.32 \times 50}{2\pi \times 2.45 \times 10^9} = 7.535 \times 10^{-9} \text{ H}$
(VII)	$C_{gs \text{ external}} = C_{gst} - C_{gs \text{ mos}} = 1.25 \times 10^{-12} - 287.75 \times 10^{-15} = 962.255 \text{ fF}$	(XV) $C_m = \frac{1}{\omega_0^2 L_m} \times \frac{Q^2}{Q^2 + 1} = \frac{1}{(2\pi \times 2.45 \times 10^9)^2 \times 7.535 \times 10^{-9}} \times \frac{2.32^2}{2.32^2 + 1} = 472.29 \text{ fF}$
(VIII)	$L_g = \frac{1}{\omega_0^2 C_{gs \text{ ext}}} - L_s = \frac{1}{(2\pi \times 2.45 \times 10^9)^2 \times 1.25 \times 10^{-12}} - 2 \times 10^{-9} = 1.37 \times 10^{-9} \text{ H}$	

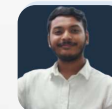


Low Noise Amplifier

Schematic Design

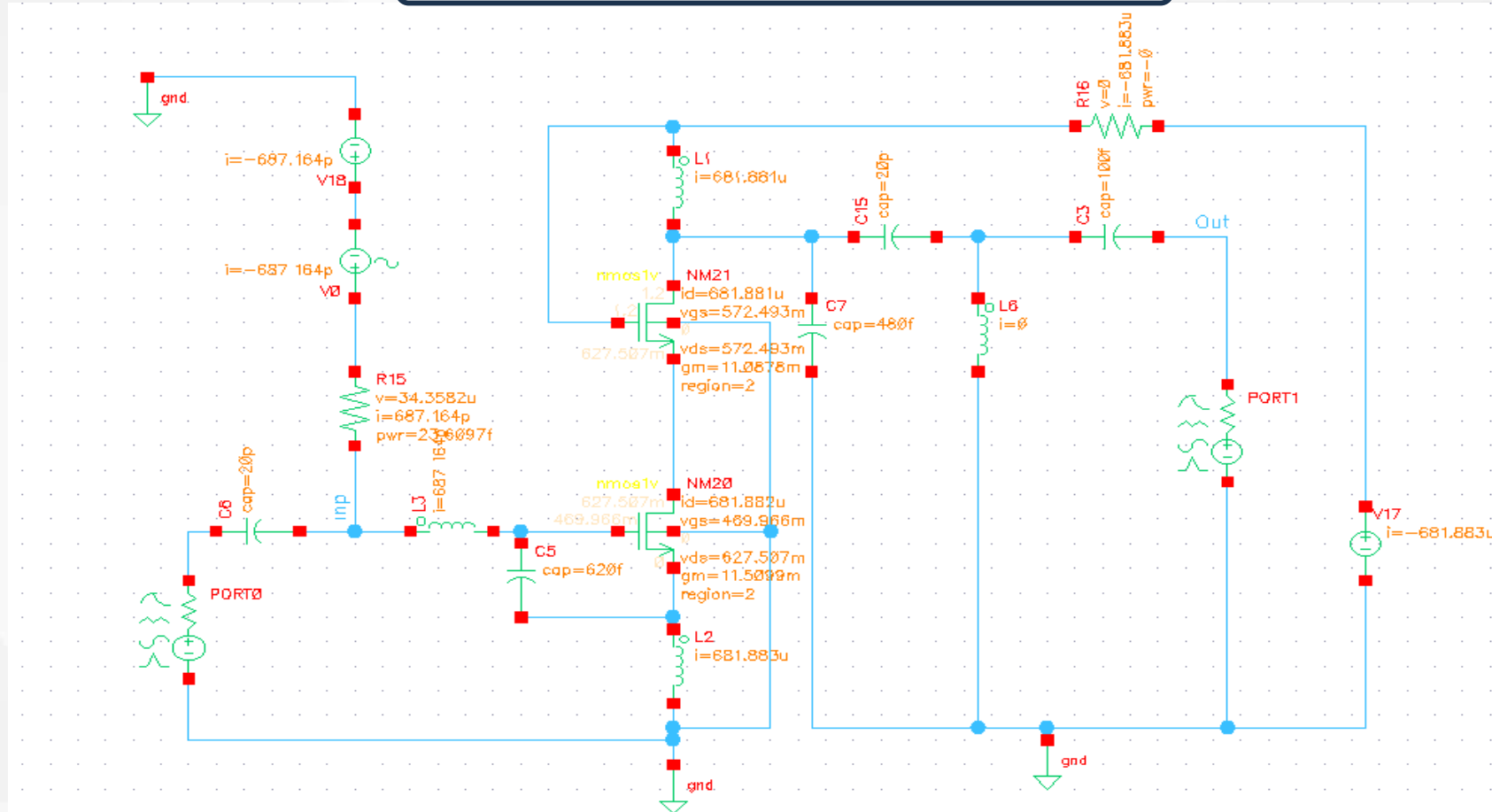

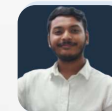 Power Consumption
 $= 681\mu A * 1.2V = 0.82mW$




Suvom Karmakar
021 221 027





Low Noise Amplifier

AC Analysis

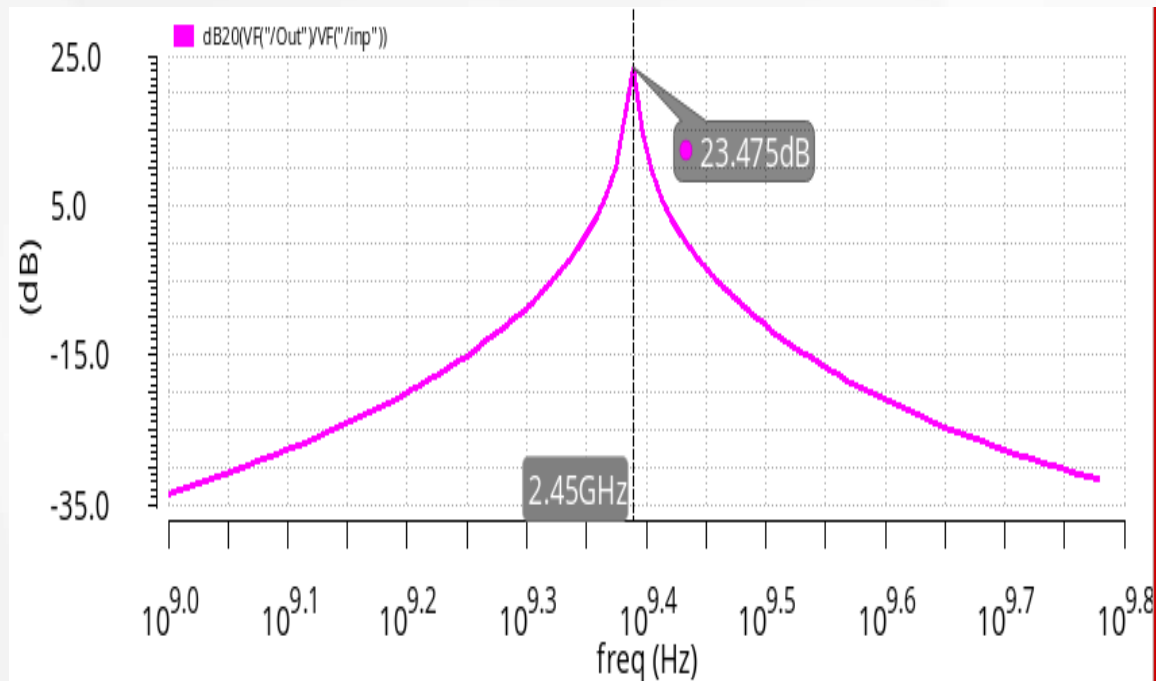

Stability Factor & NF Analysis

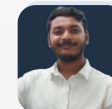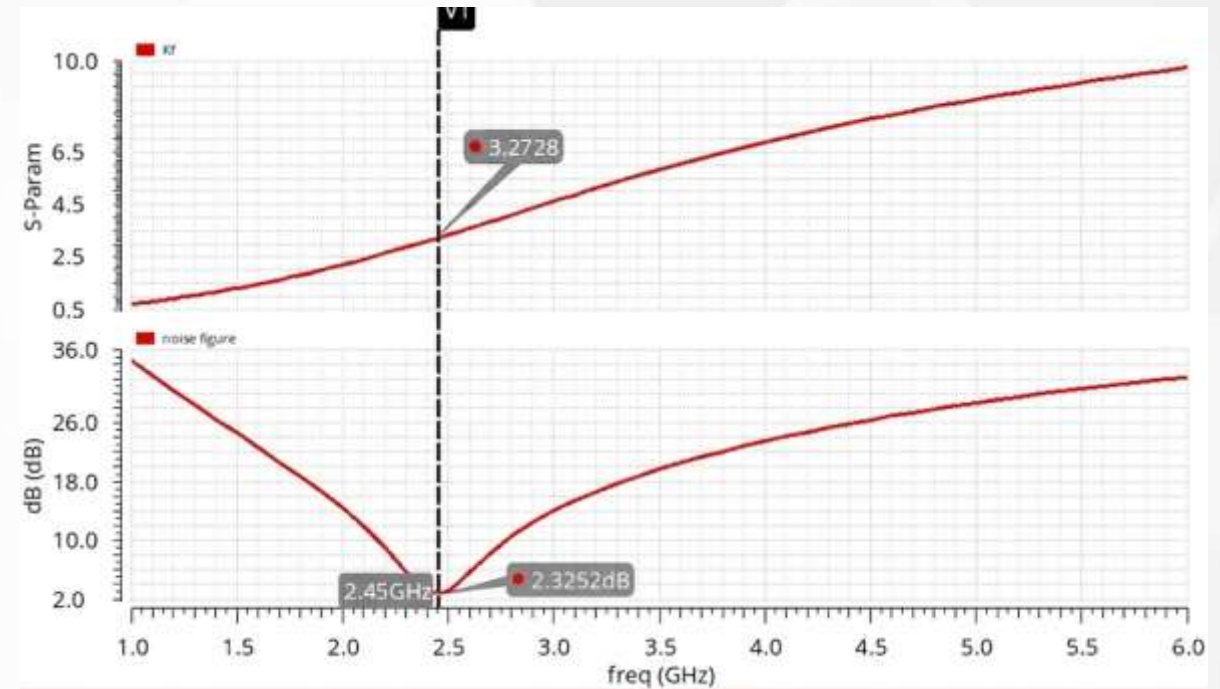


Suvom Karmakar
021 221 027



Low Noise Amplifier



Transient Analysis

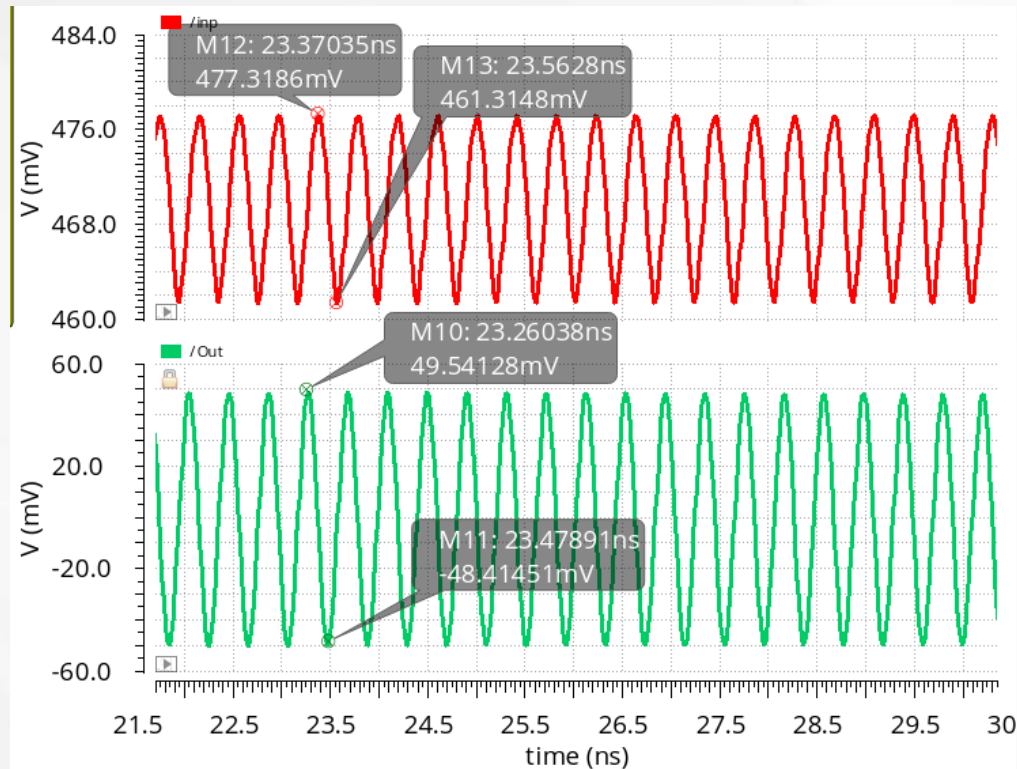

$$A_v = 20 \log_{10} \left(\frac{(49.541 + 48.414) \text{mV}}{(477.318 - 461.314) \text{mV}} \right)$$

$$A_v = 16.3 \text{ dB}$$

S-Parameter Analysis

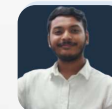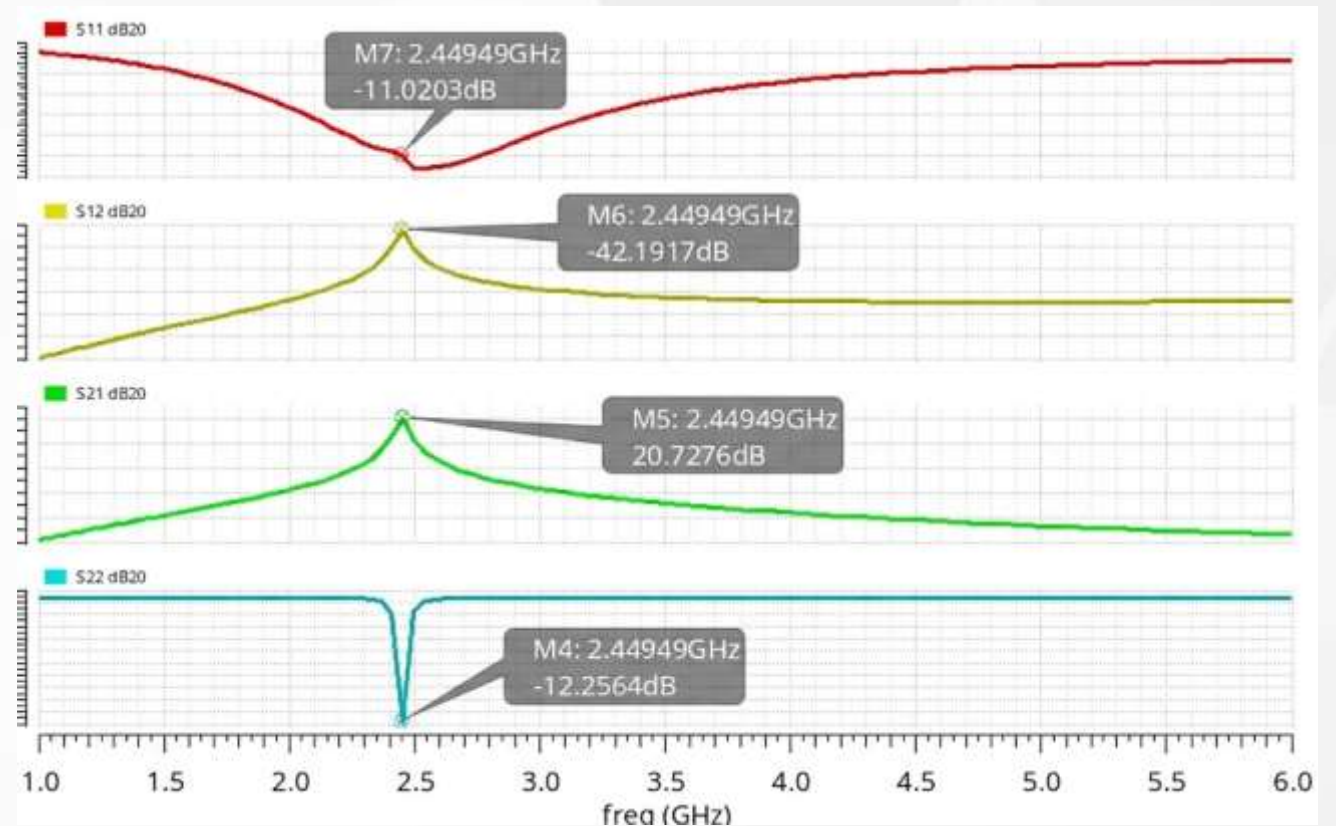


Suvom Karmakar
021 221 027



Low Noise Amplifier


Performance Summary:

Design Metric	Measurement	Simulation Result	Requirement
Input Return Loss	S11 at 2.45 GHz	-11.03 dB	≤ -10 dB
Forward Gain	S21 at 2.45 GHz	20.72 dB	15 dB -20 dB
Maximum Gain	Gain at 2.45 GHz	23.47 dB	≥ 15 dB
Noise Figure	NF at 2.45 GHz	2.32 dB	<3.0 dB
Output Return Loss	S22 at 2.45 GHz	-12.25 dB	≤ -10 dB
Reverse Isolation	S12 at 2.45 GHz	-42.19dB	≤ -25 dB

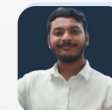

Band Pass Filter

Schematic Design

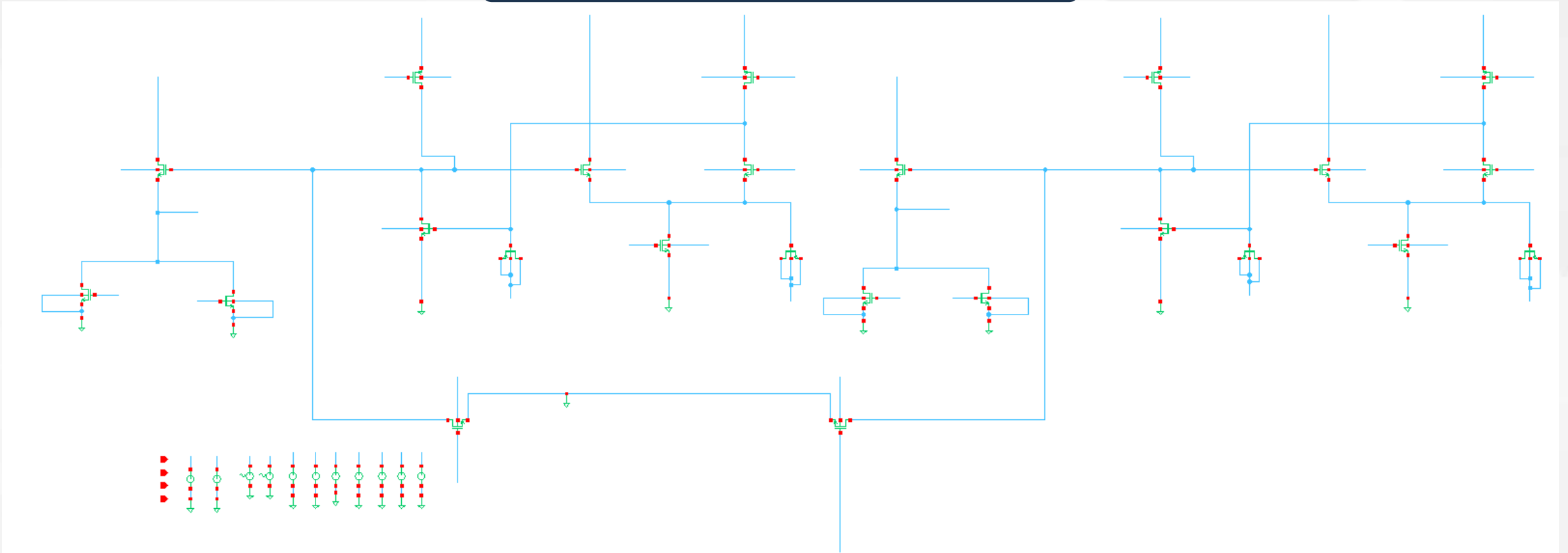


Power Consumption = 1.63mW



Tahman Hossain
021 221 099



Band Pass Filter

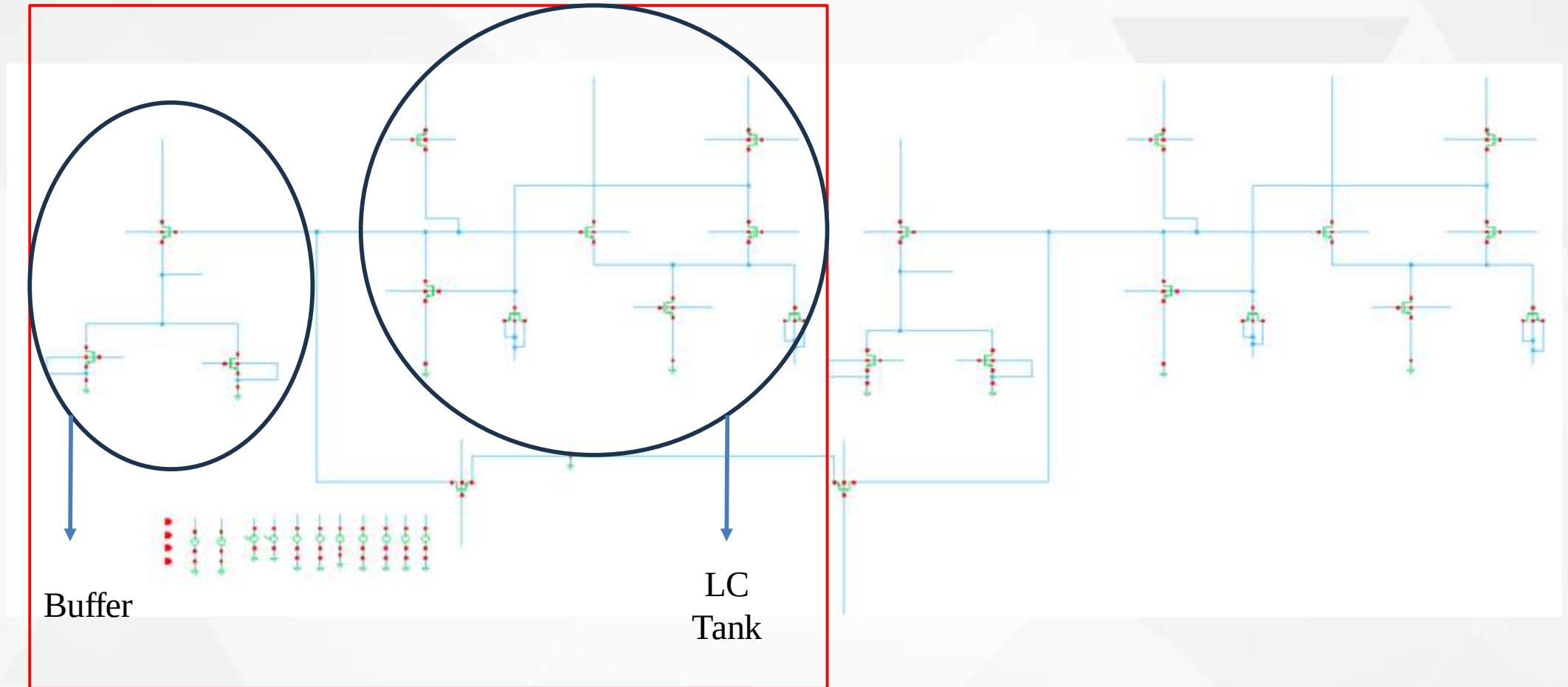


Tahman Hossain
021 221 099




Band Pass Filter

Center Frequency

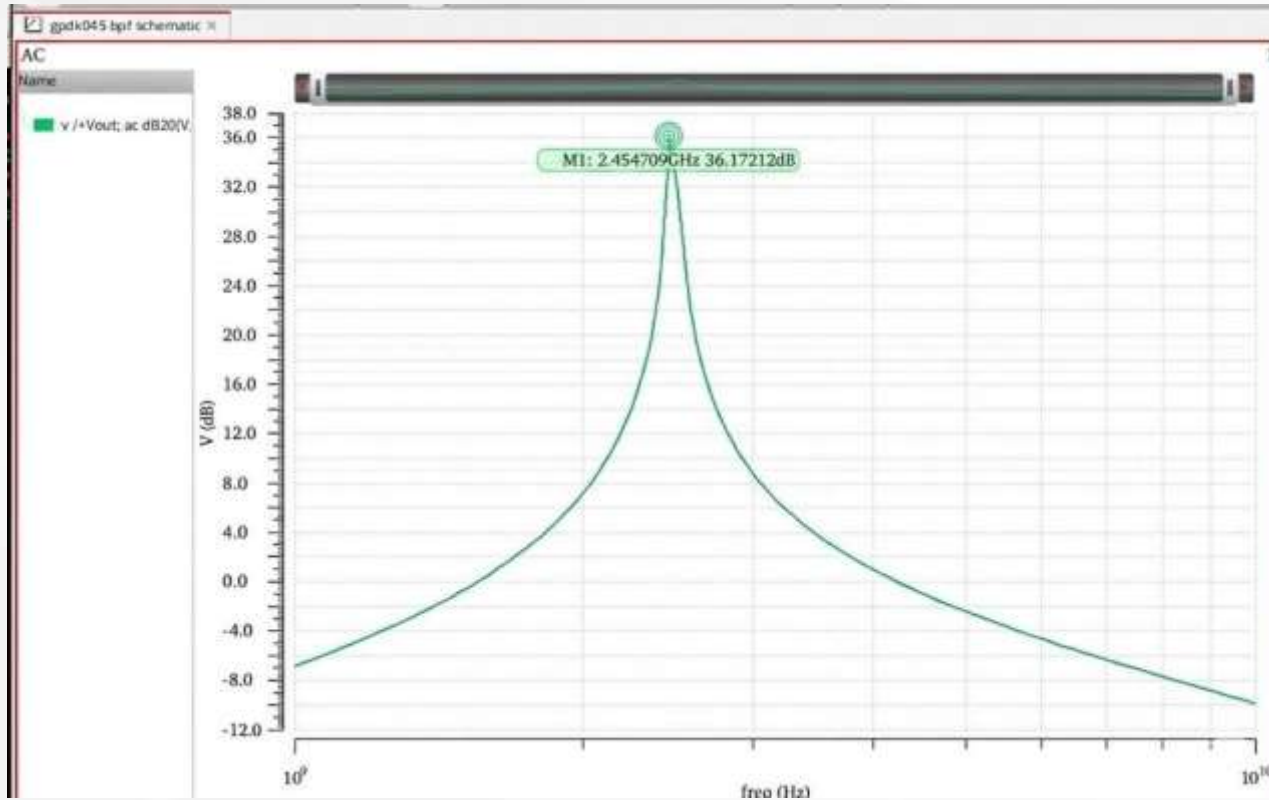

3 dB Point

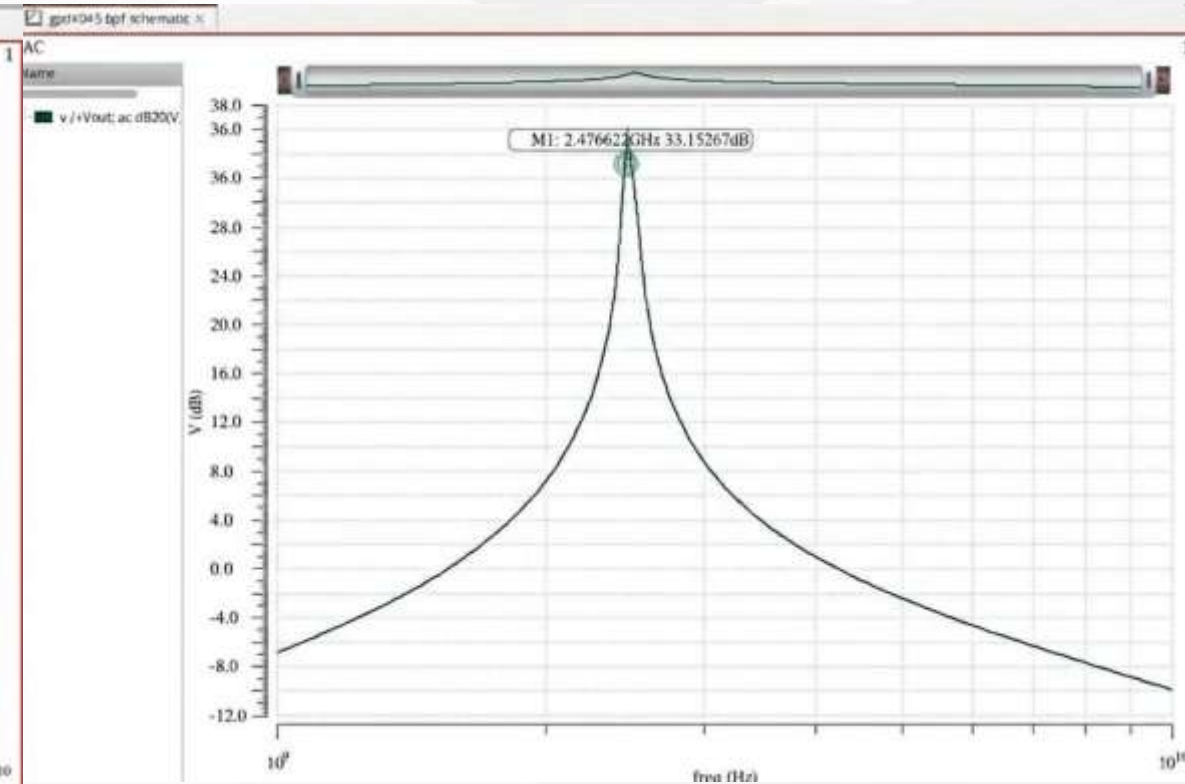


Tahman Hossain
021 221 099



Band Pass Filter

Transient & DFT Analysis

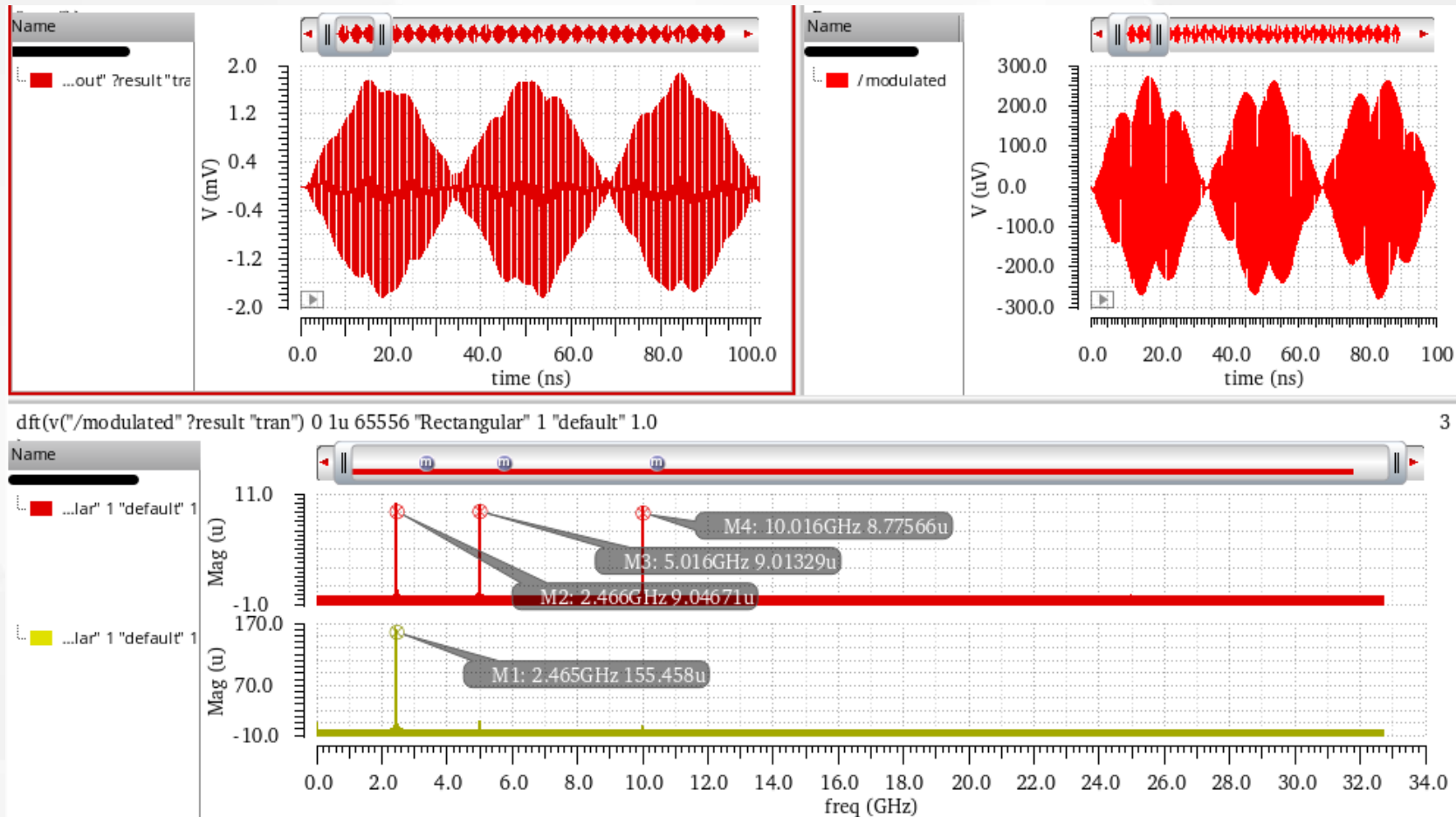


Tahman Hossain
021 221 099




RF Receiver

Integration of RF Blocks

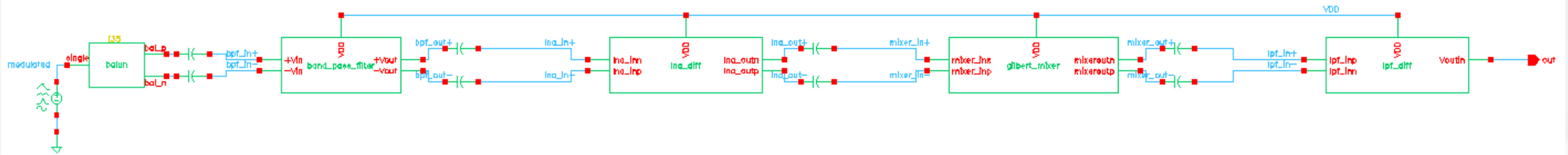

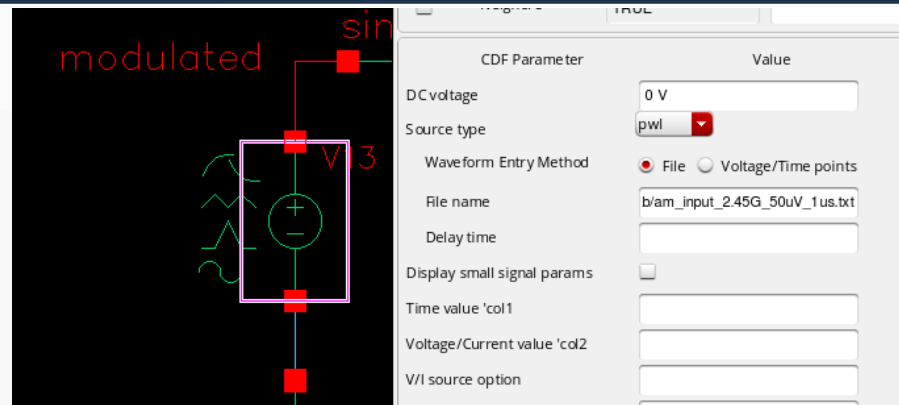Uploading MATLAB Generated Modulation Signal




Tahman Hossain
021 221 099



RF Receiver

DSB-SC Transient analysis

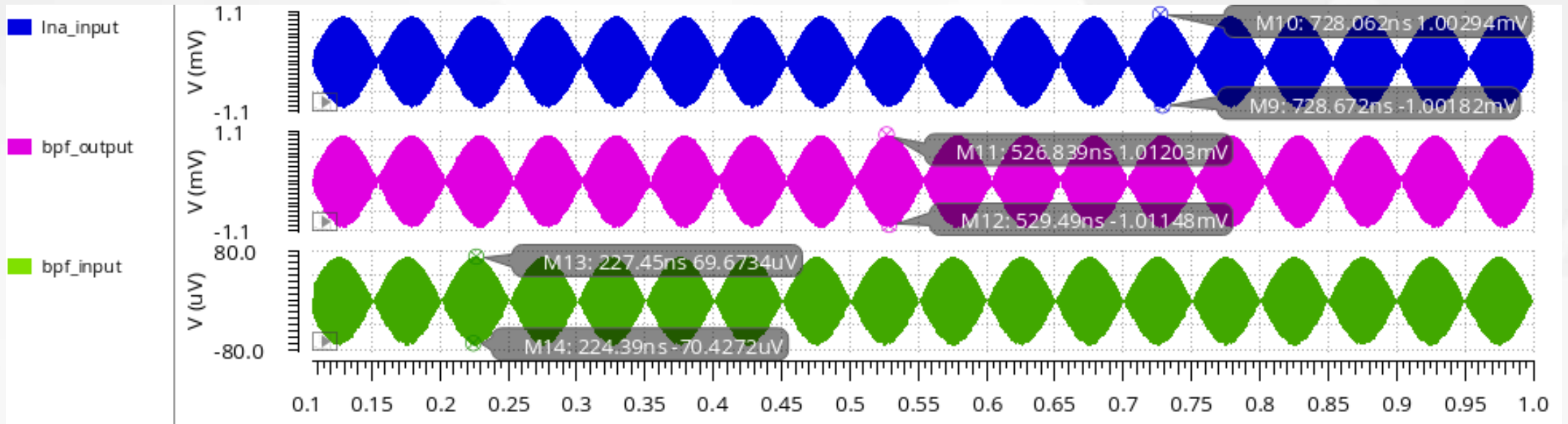

- Message signal - 10MHz
- Carrier frequency - 2.45GHz
- Amplitude - 50uV




Sazzad Hossen
021 221 026



RF Receiver

DSB-SC Transient analysis (cont.)

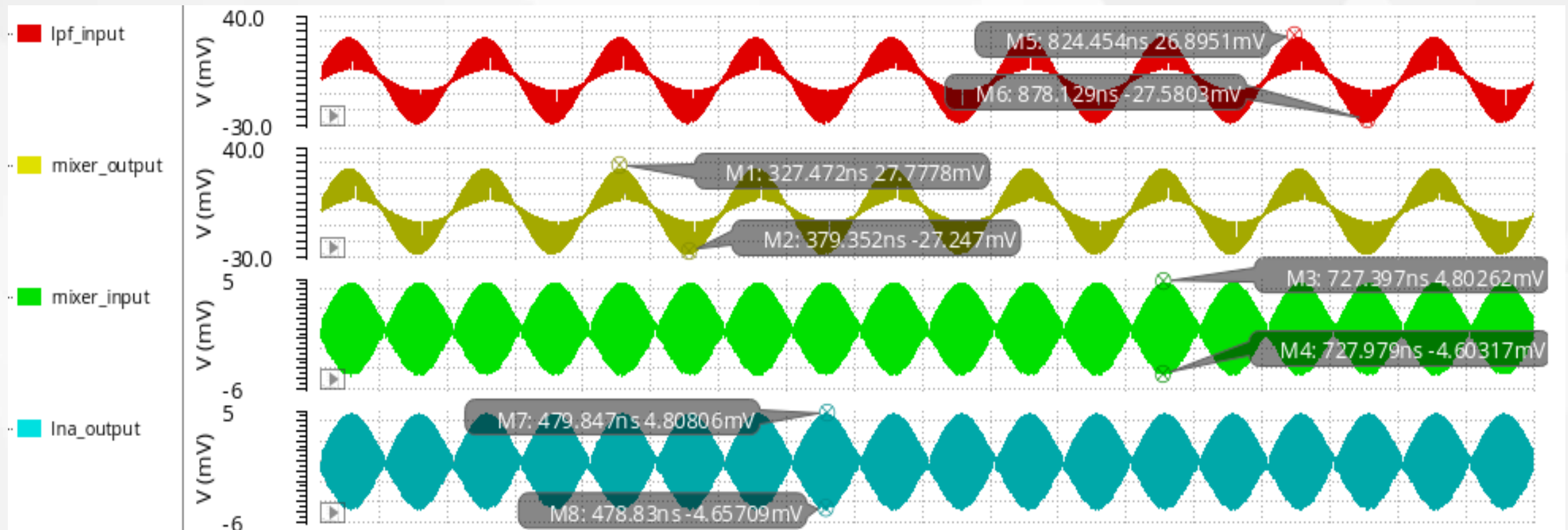


Sazzad Hossen
021 221 026



RF Receiver

DSB-SC Transient analysis (cont.)

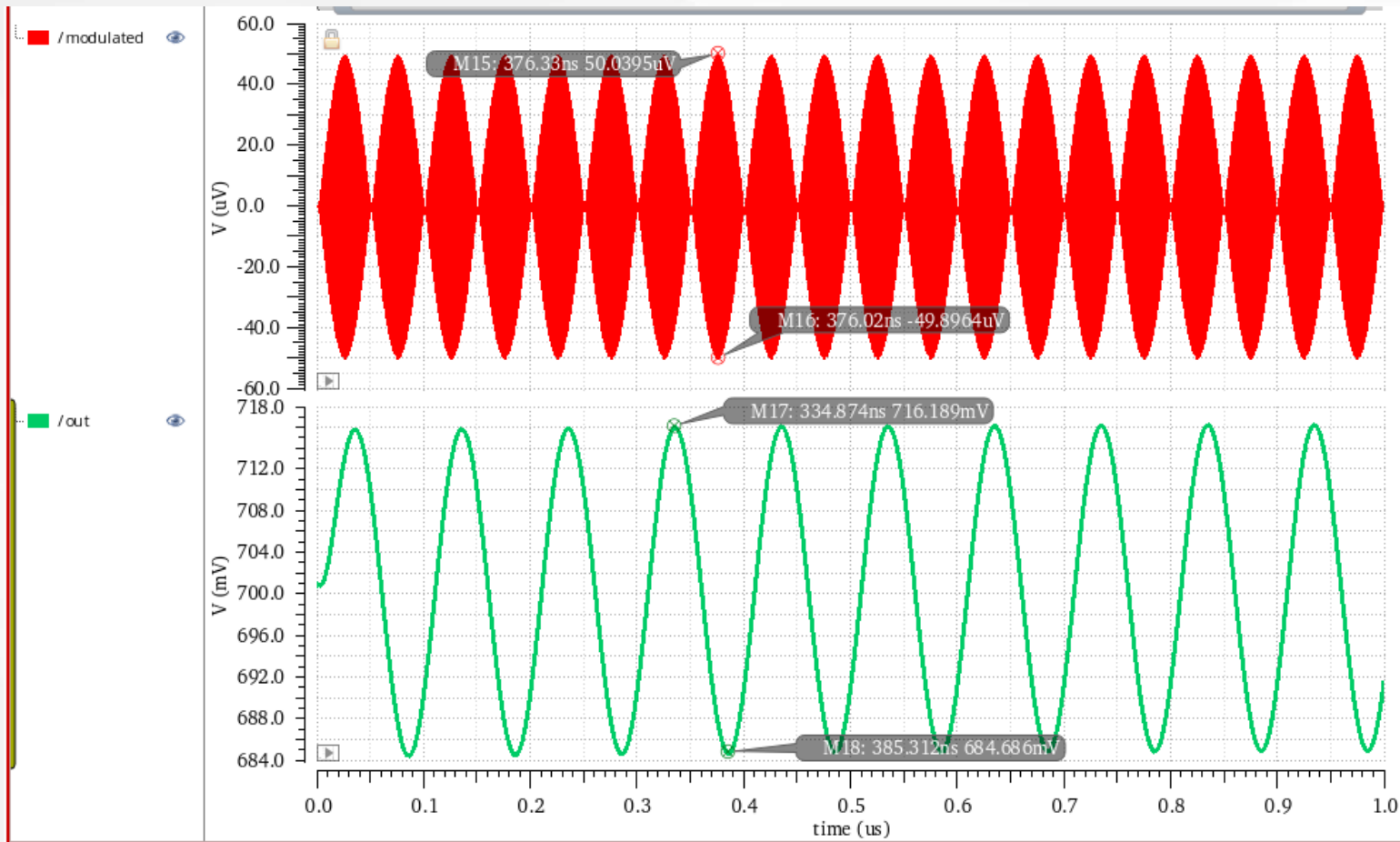

$$A_v = \frac{V_{out}(peak_to_peak)}{V_{in}(peak_to_peak)}$$
$$= \frac{31.5 \times 10^{-3}}{100 \times 10^{-6}} = 320$$

$$A_v = 50 \text{ dB}$$





Sazzad Hossen
021 221 026



RF Receiver

DSB-SC DFT Analysis

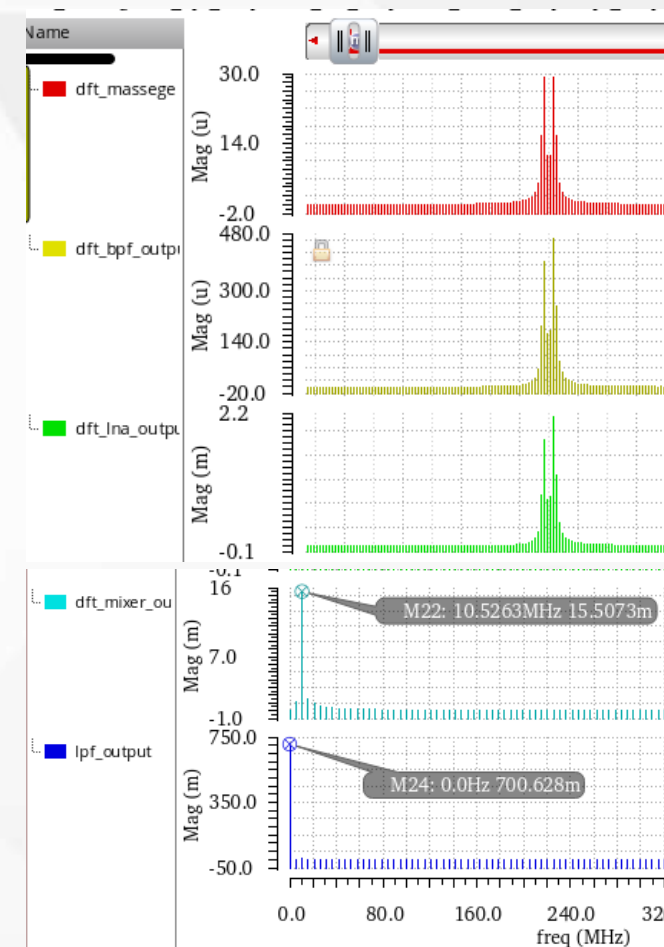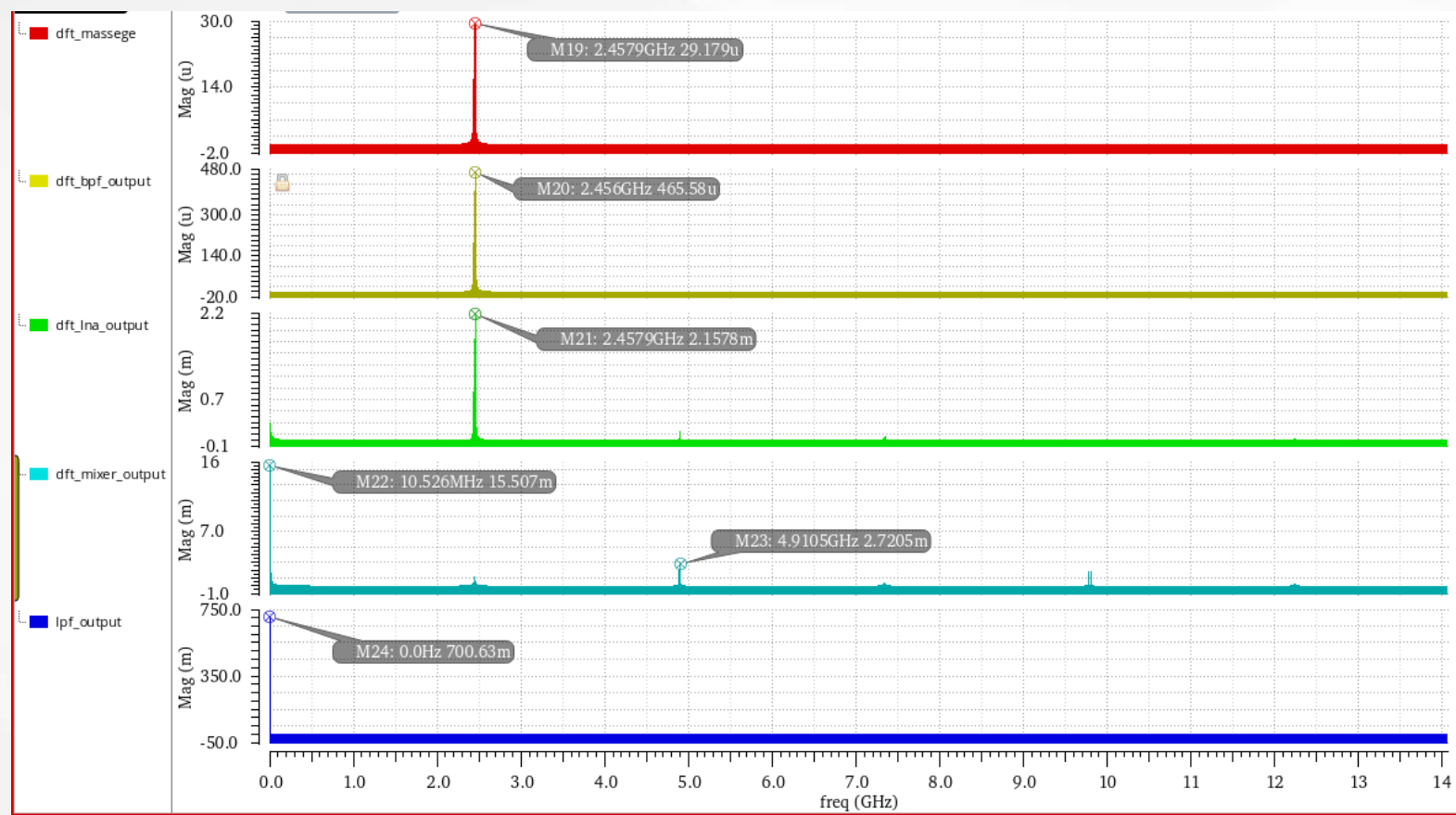


Sazzad Hossen
021 221 026



RF Receiver


PSD Analysis

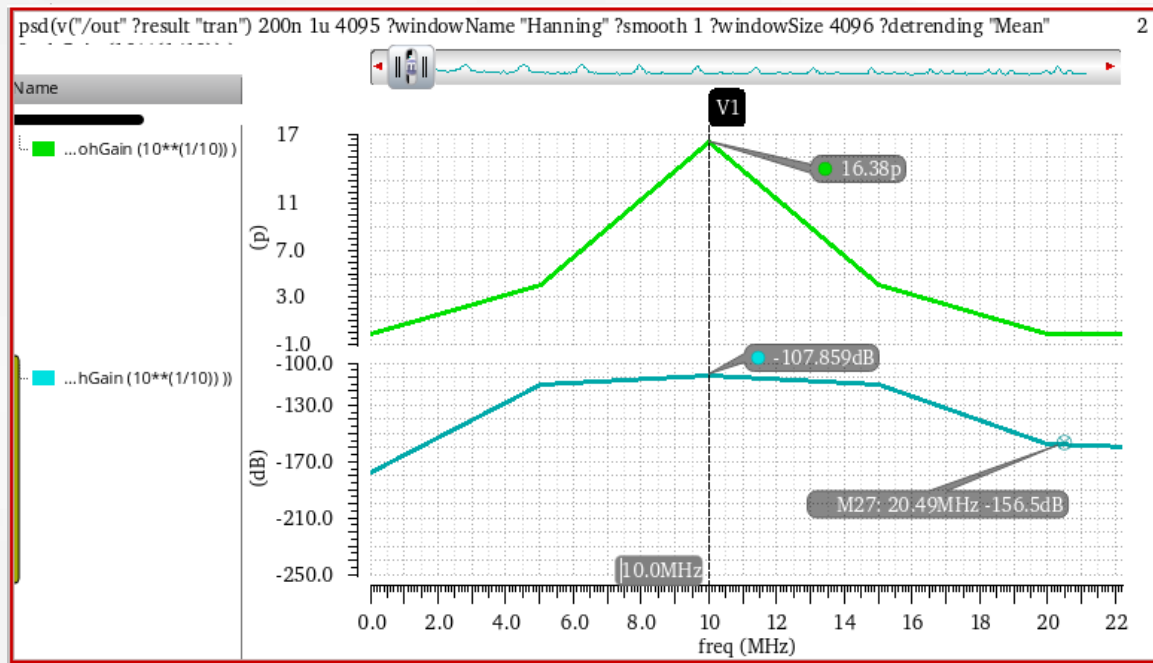

$$SNR_{dB} = P_{signal} - P_{noise}$$

$$SNR_{dB} = (107.85dB - 156.5 dB) = 49 dB$$

Linearity Analysis

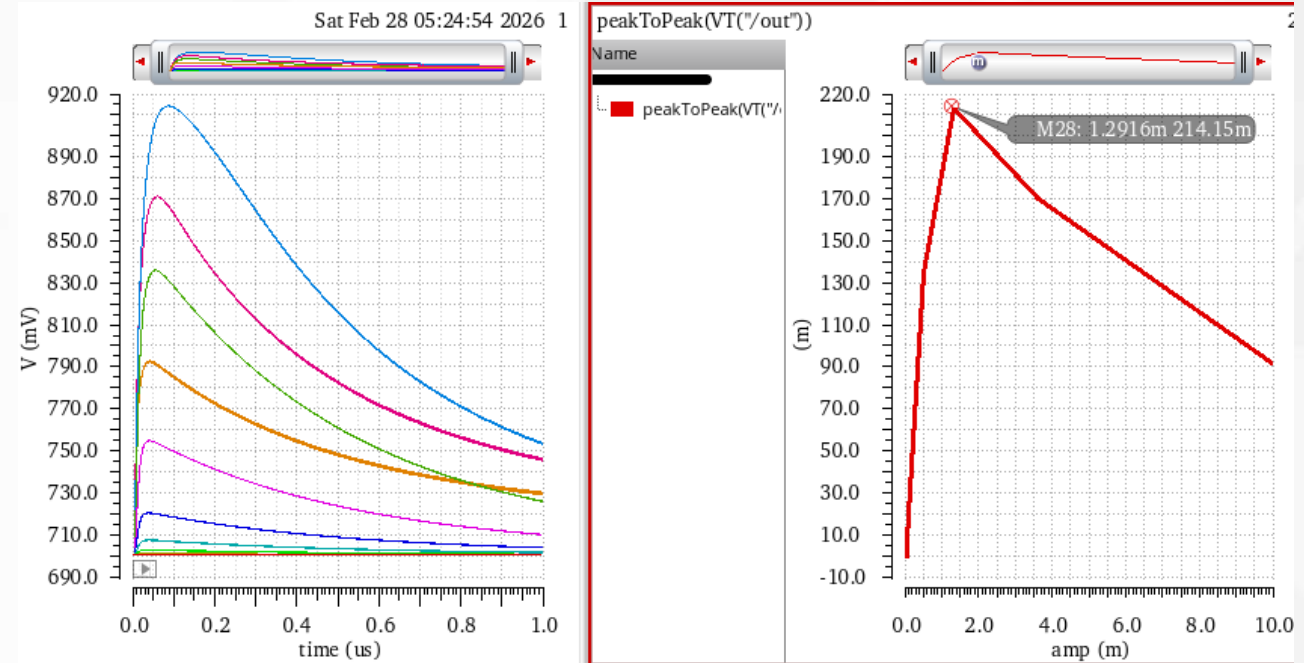

Linearity range : 1uV – 1.3mV




Sazzad Hossen
021 221 026



RF Receiver

FDM Transient Analysis

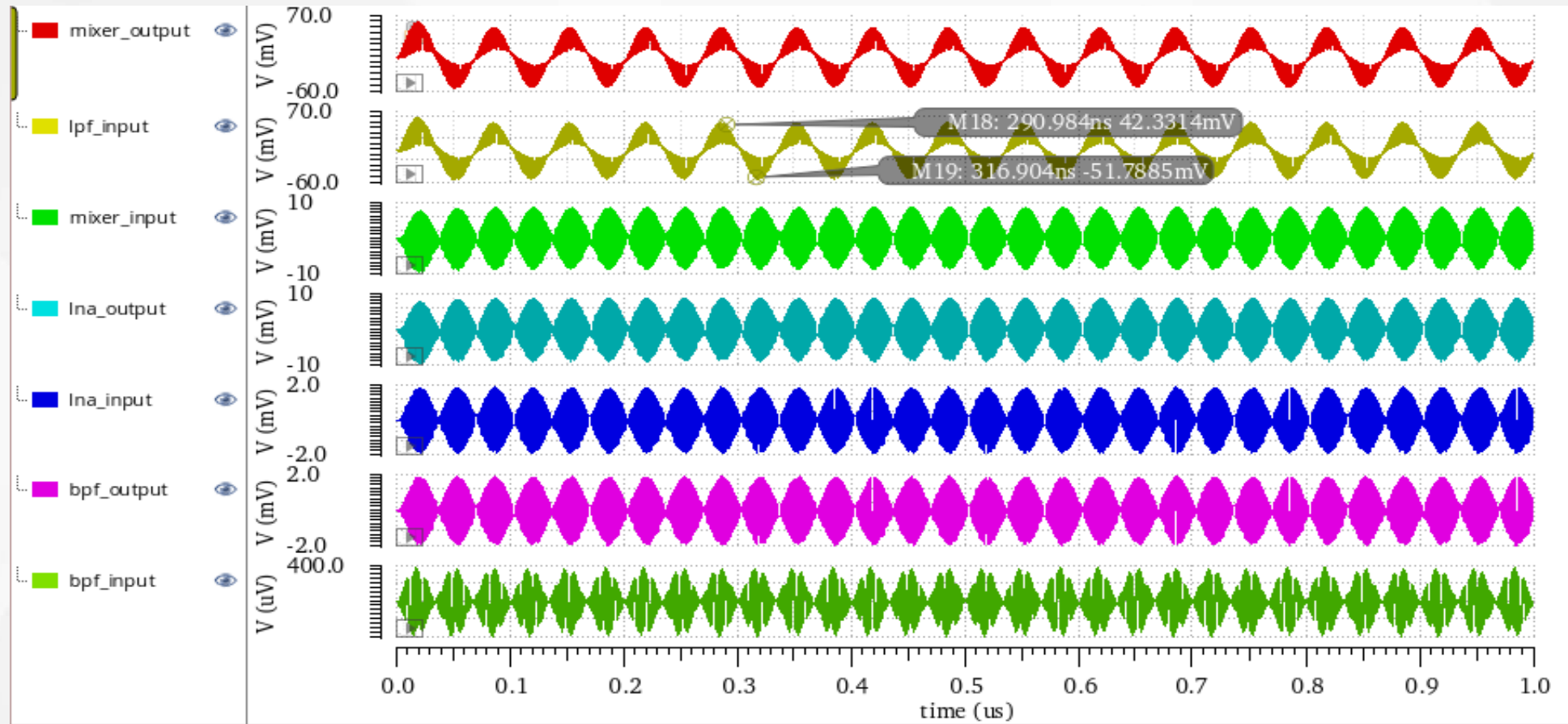

- Message signal – 15MHz
- Carrier frequency – 2.45GHz, 5GHz, 10GHz
- Amplitude – 100uV




Sazzad Hossen
021 221 026



RF Receiver

FDM DFT Analysis

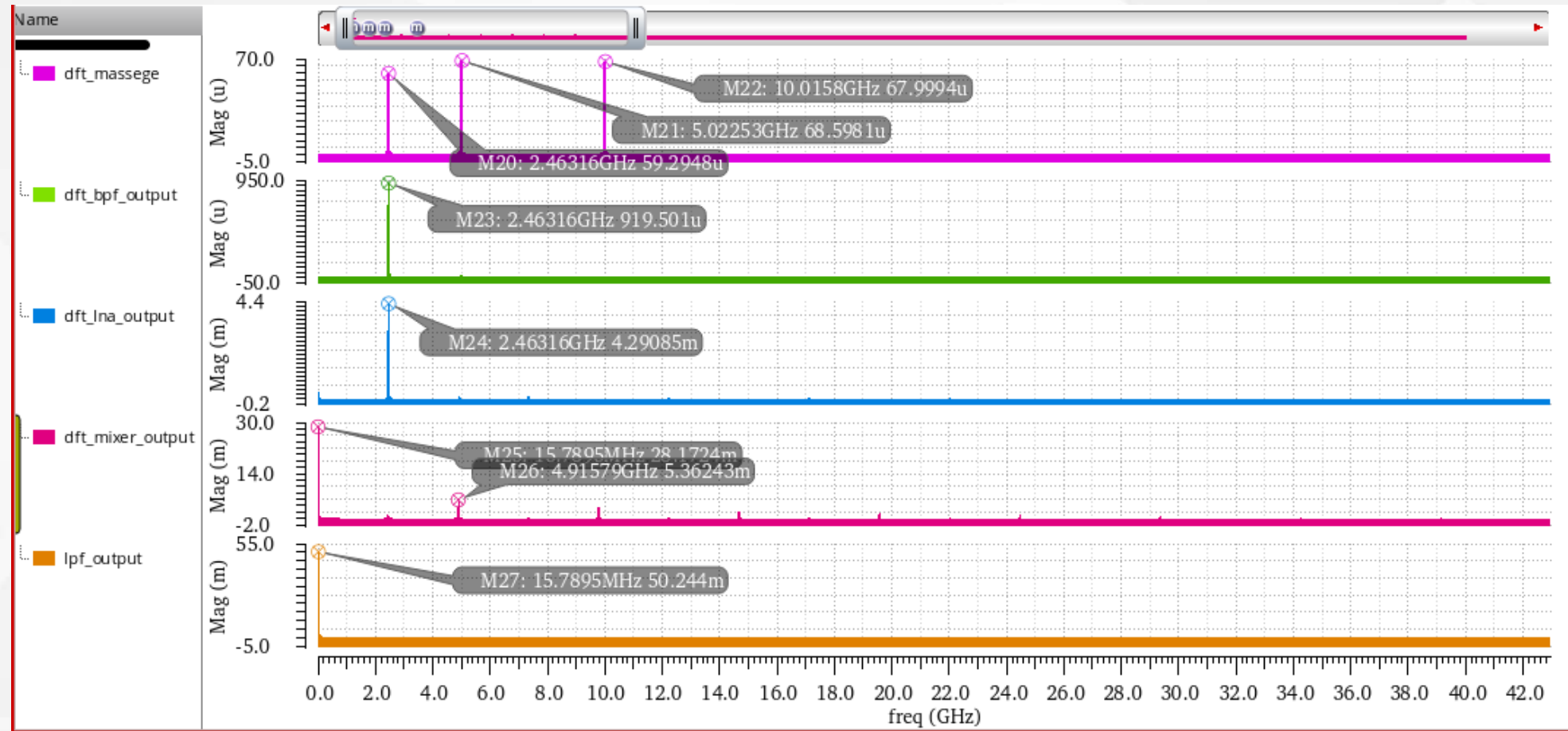


Sazzad Hossen
021 221 026



RF Receiver

FDM Transient Analysis (cont.)

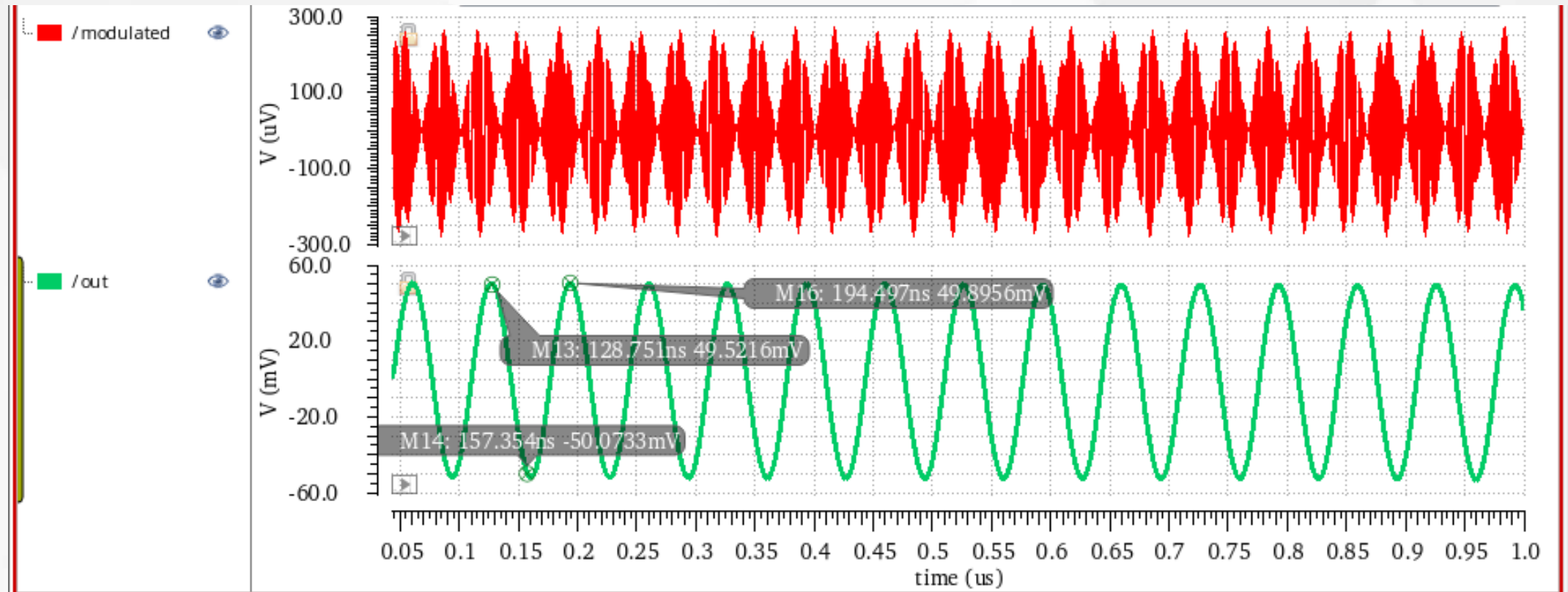

Sazzad Hossen
021 221 026




RF Receiver

Output Summary



6mW

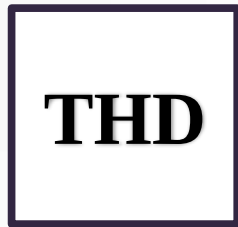

1.3%



49 dB

Future Direction

Integration of Advanced Blocks



Physical Layout Design



Further Power Optimization




Sazzad Hossen
021 221 026



RF Receiver

I/Q (In-phase & Quadrature) Structure

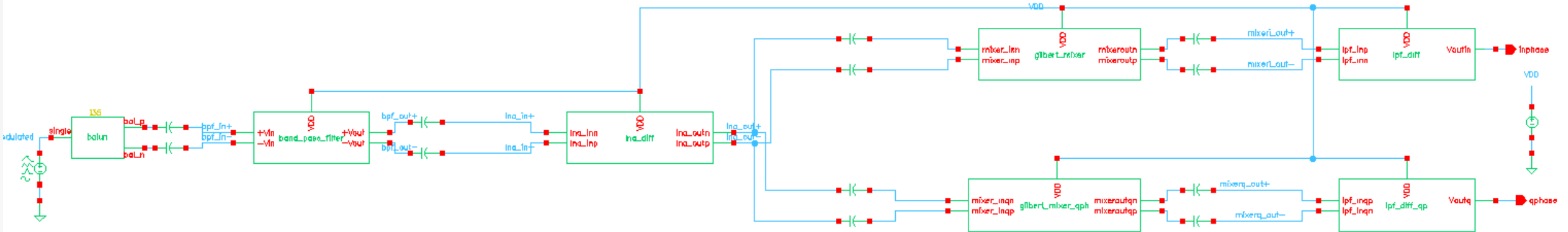

Power Consumption of 8.79mW





Sazzad Hossen
021 221 026



RF Receiver

Single Tone Test

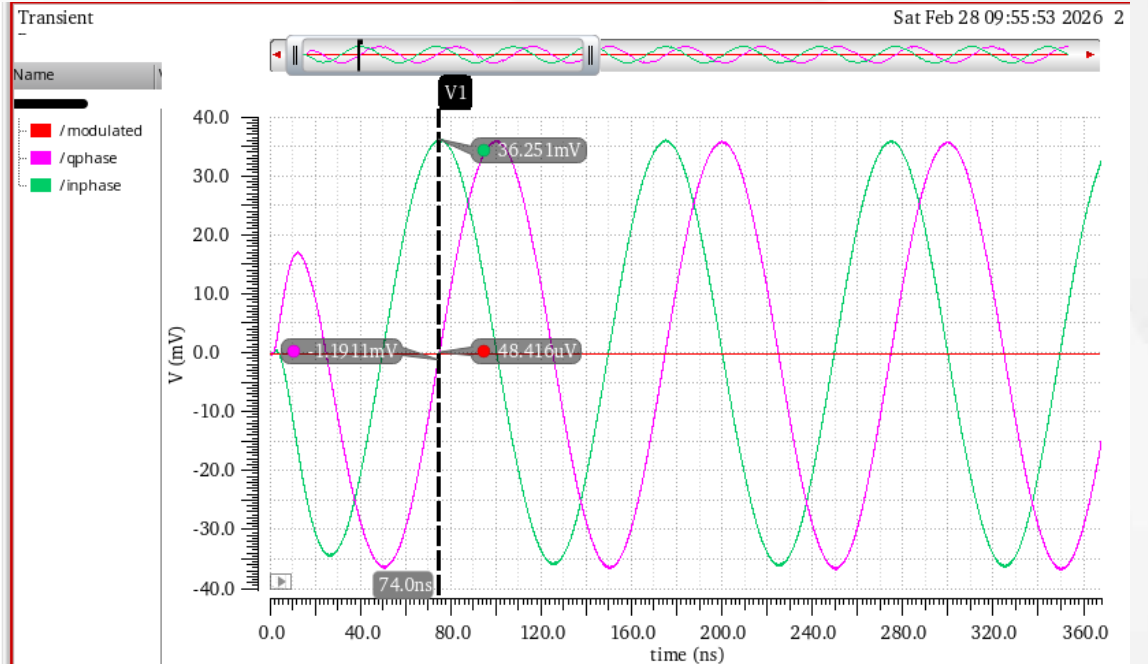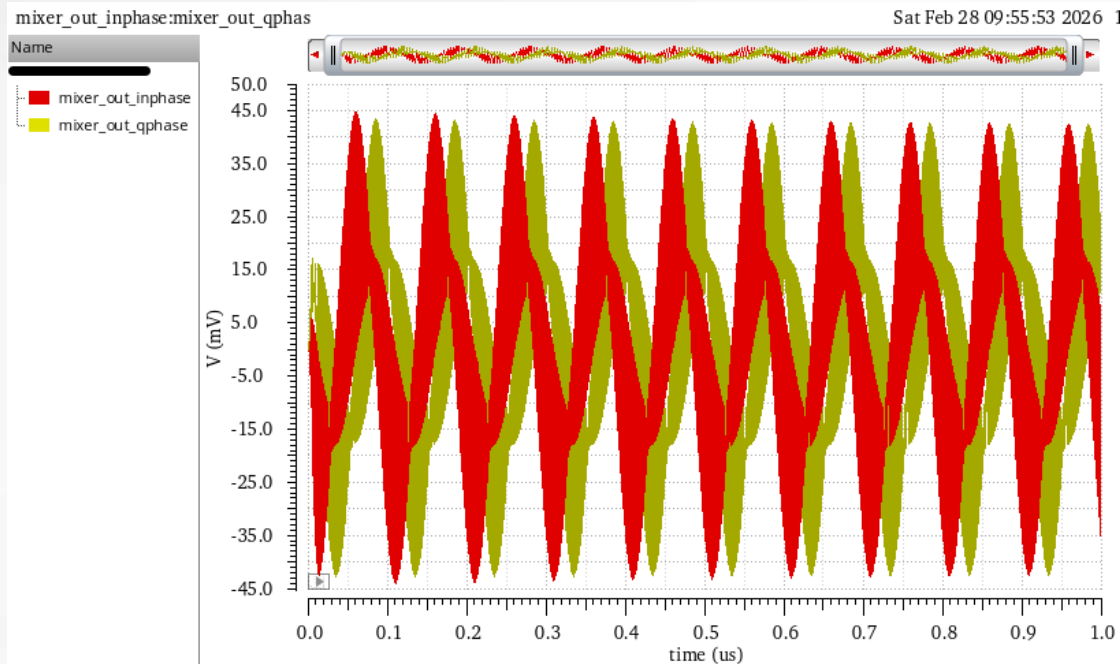


Sazzad Hossen
021 221 026



RF Receiver

Lissajous pattern

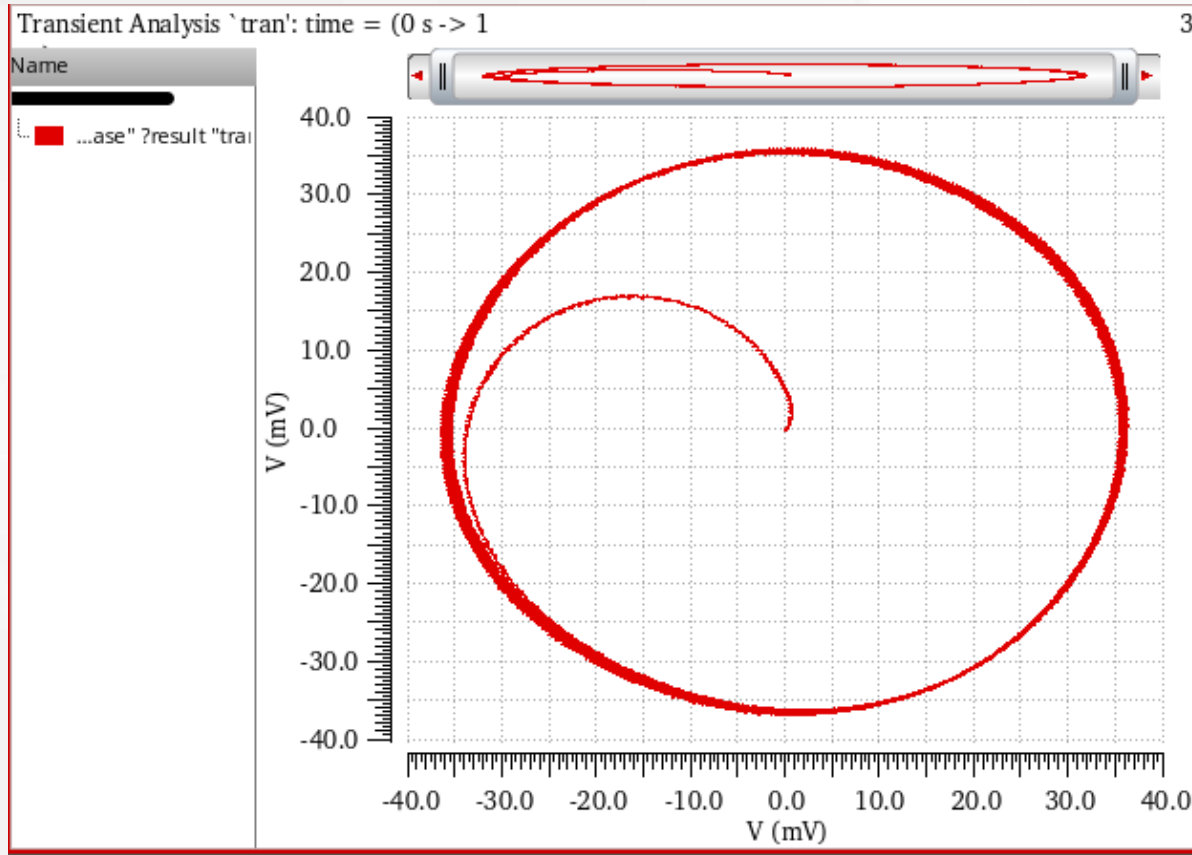

- ❑ The perfect circular Lissajous pattern confirms 0 dB gain mismatch and 0 phase error between the I and Q channels.



Sazzad Hossen
021 221 026



Project Attributes

 Program Outcomes (POs)

POs

PO2: Problem Analysis

PO3: Design/Development of Solutions

PO4: Investigation

PO5: Modern Tool Usage

PO6: Engineer and Society



Knowledge Profile (K)

K's

☐ K01

☐ K03

☐ K04

☐ K05

☐ K08



Sustainability & SDG Alignment

SDG

SDG 4 Quality Education

SDG 7 Affordable and Clean Energy

SDG 9 Industry, Innovation, and Infrastructure

SDG 12 Responsible Consumption and Production



Sazzad Hossen
021 221 026



Communication & Co-ordination

Weekly Meetings

Regular check-ins with supervisors to discuss progress, address challenges, and plan next steps.

Work Division

Specific responsibilities for BPF, LNA, Mixer, and LPF design, with cross-support for testing and integration.

Documentation

Comprehensive technical reports and design logs to ensure knowledge transfer and traceability.

Key Takeaways

- Robust RF receiver design for ISM band applications.
- Strong alignment with engineering program outcomes and knowledge profiles.



Comparison Table

Category	Parameter	[1]	[2]	[3]	[4]	[5]	[6]	This Work
Process	Technology (nm)	-	180	600	180	180	40	45
	Supply Voltage (V)	-	1.5	3	1.8	1.5	1.1	1.2
System	Frequency (GHz)	2.4	24	2.4	24	2.42	-	2.45
	Total Gain (dB)	35	14.5	12 - 20	25	-	-	50
	Total Power (mW)	40	45	100	25.2	-	-	6.261
LNA	Gain (dB)	-	15	14	14.7	-	-	23.03
	NF (dB)	-	6	3.5	4.3	-	-	2.4
	Topology	-	Common Gate	Common Source Cascode	Transformer-Coupled	-	-	Common Source Inductive Degeneration
Mixer	Conv. Gain (dB)	-	12.5	10	8.7	-	-	
	Type	-	Active Gilbert Cell	Active Gilbert Cell	Current-Bleeding Mixer	-	-	Active Gilbert Cell
BPF	Bandwidth (MHz)	-	-	-	-	38	-	20-100 (Tunable)
	Power Consumption (mW)	-	-	-	-	1.3 (Single Stage)	-	1.63 (Differential)
LPF	Bandwidth (MHz)	-	-	-	-	-	20	20
	Power Consumption (mW)	-	-	-	-	-	2	0.2



Sazzad Hossen
021 221 026



Conclusion

- ✓ 2.45 GHz CMOS RF Receiver Design (45 nm).
- ✓ Reliable wireless application.
- ✓ Effective weak-signal restoration.
- ✓ Low power consumption (6.261 mW).
- ✓ Gain: 320 & THD: 1.319%
- ✓ Scalable for advanced modulation.





Thank You






Any  **Question?**



Receiver Design



AM (Transient analysis)

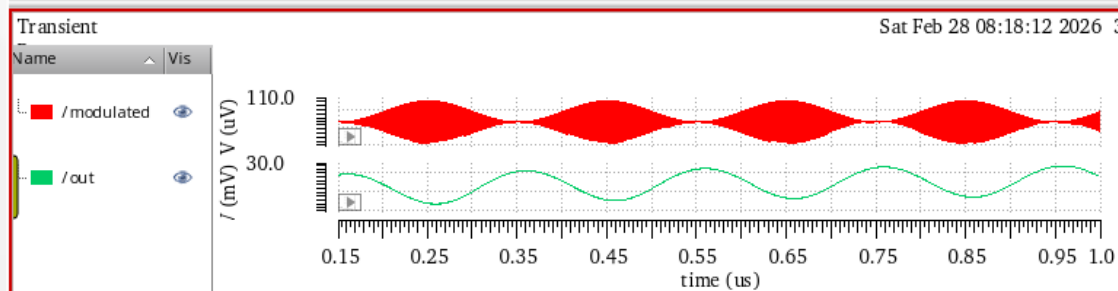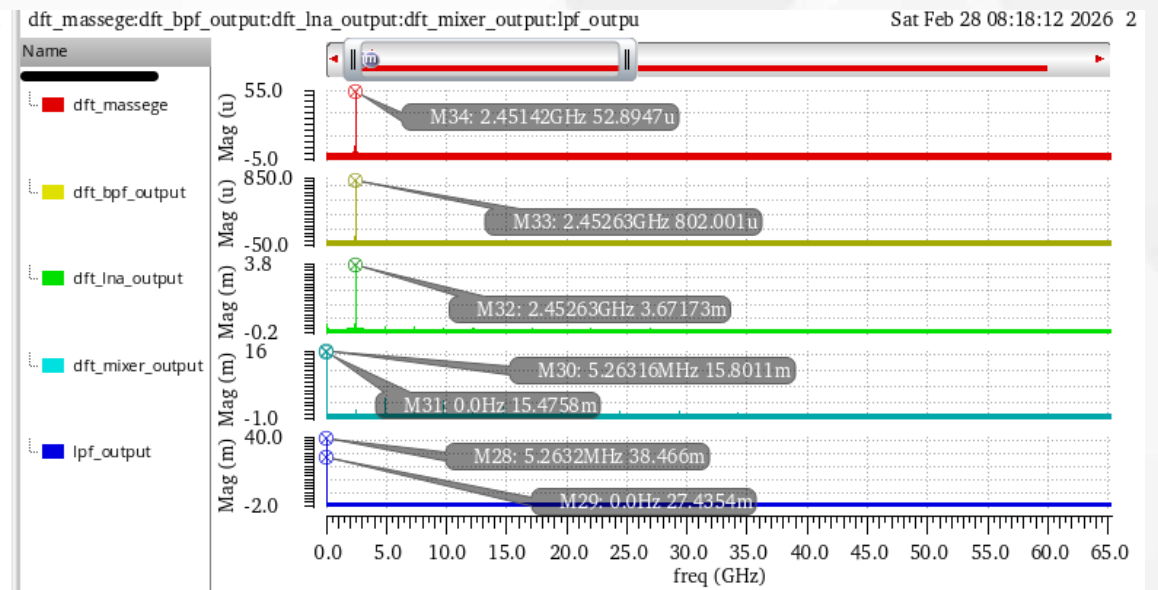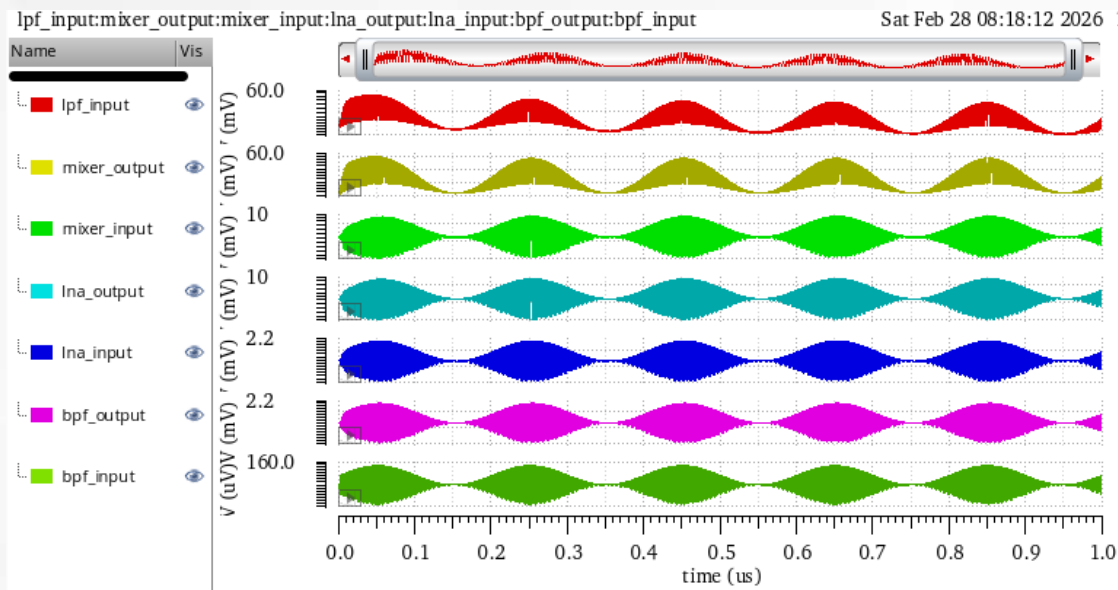Message signal – 5MHz
Carrier frequency – 2.45GHz
Amplitude – 50uV




Receiver Design


QPSK Transient Analysis

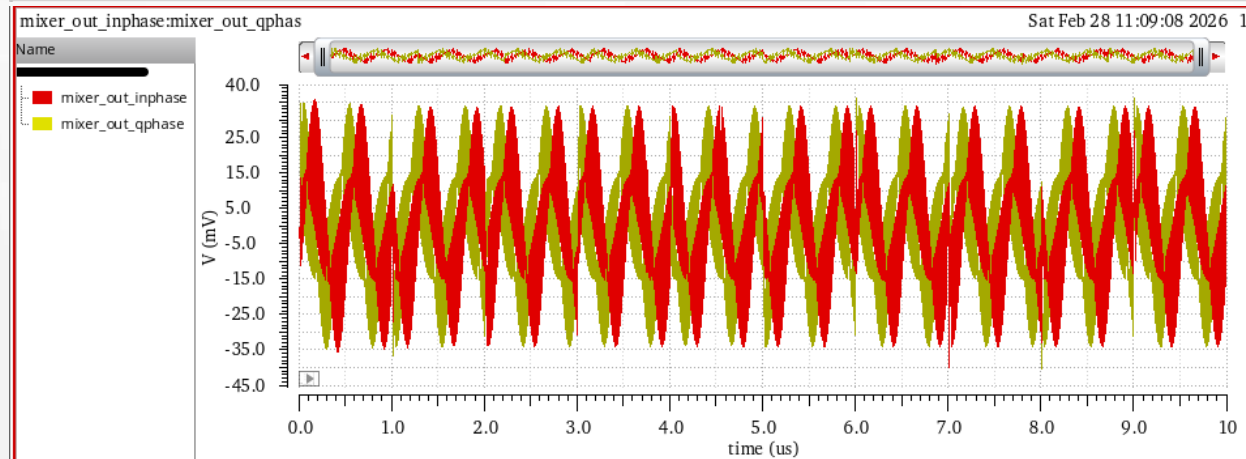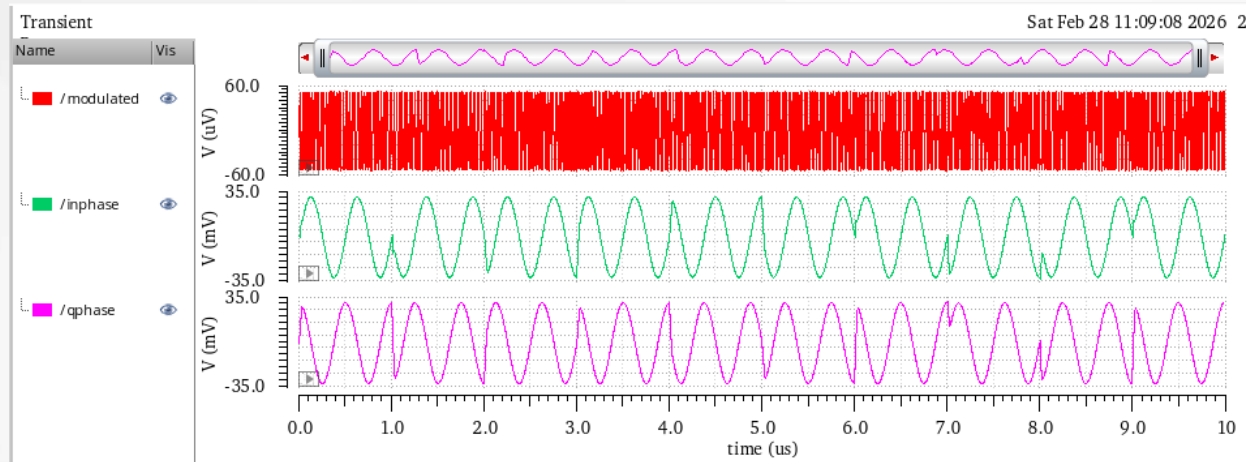

Lissajous pattern

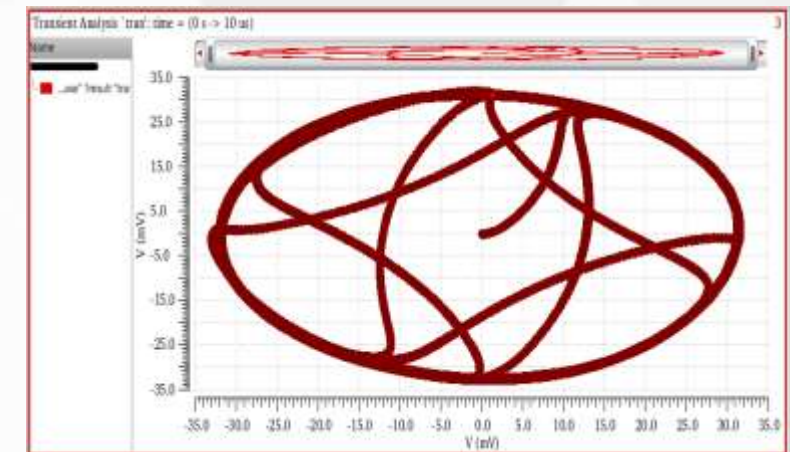


Eye Diagram

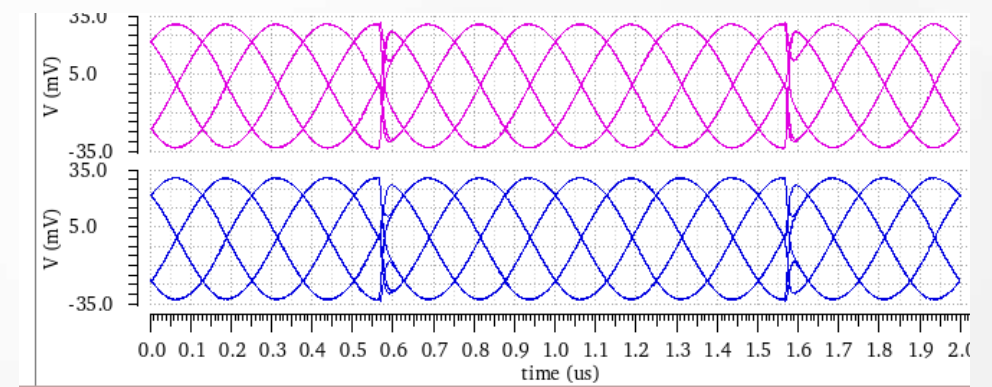


Mixer Design

Mixer schematic with Impedance matching

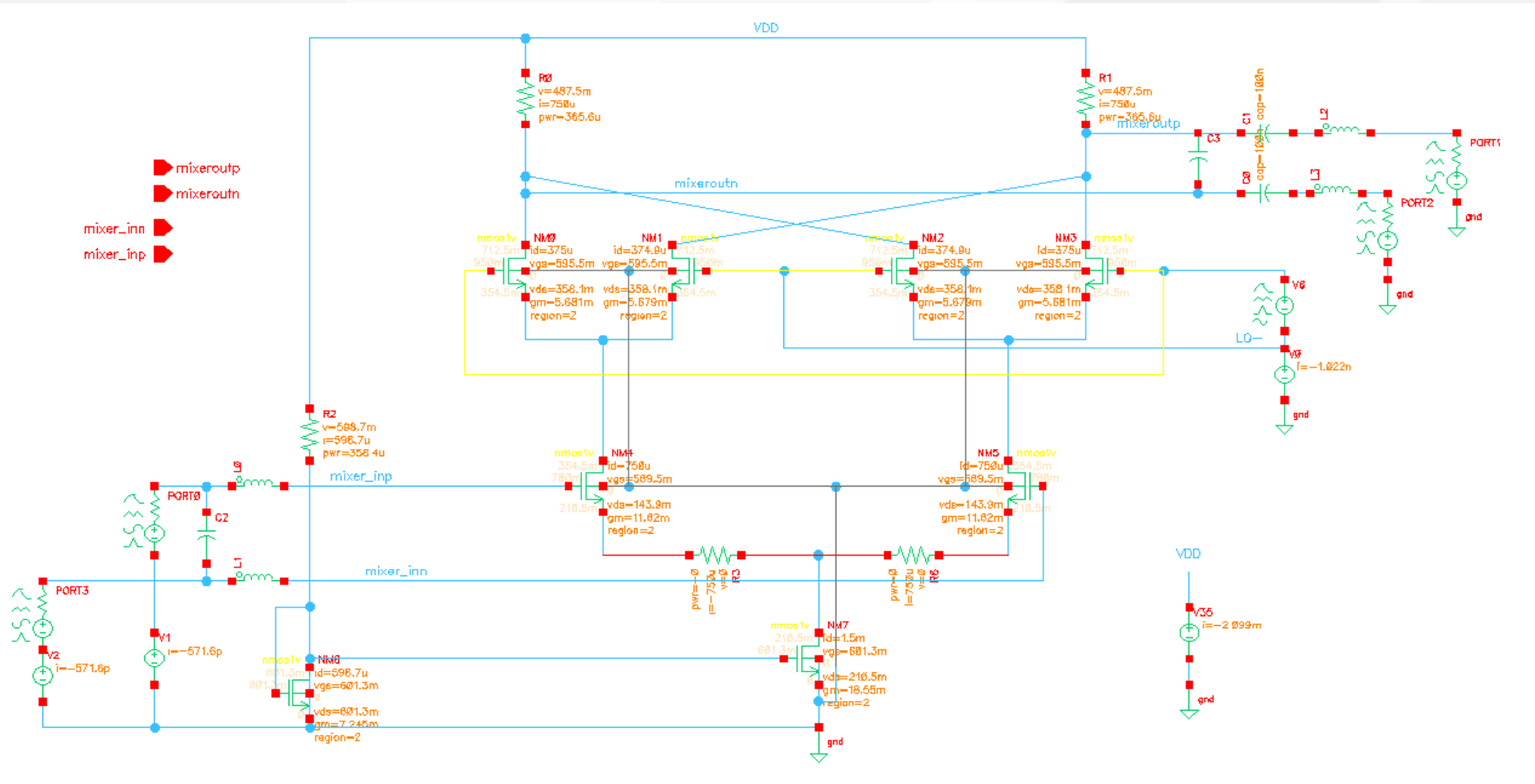


Mixer Design

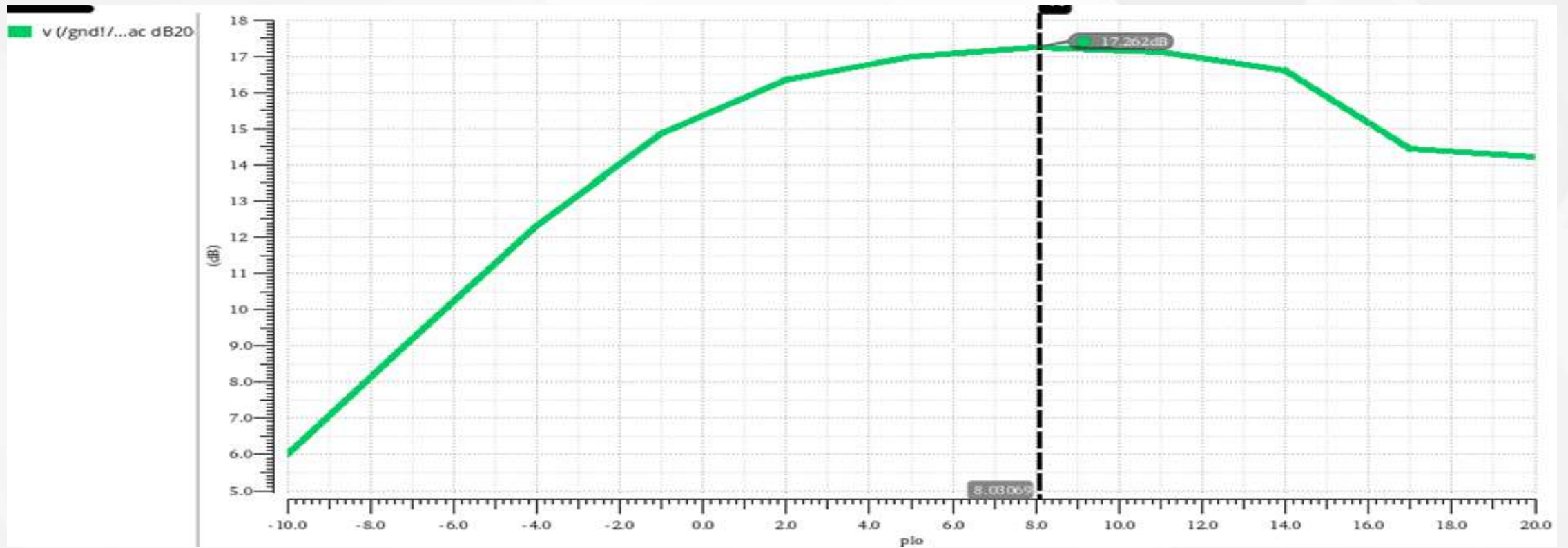Voltage Conversion Gain Vs. LO Signal Power




Mixer S- Parameter Analysis

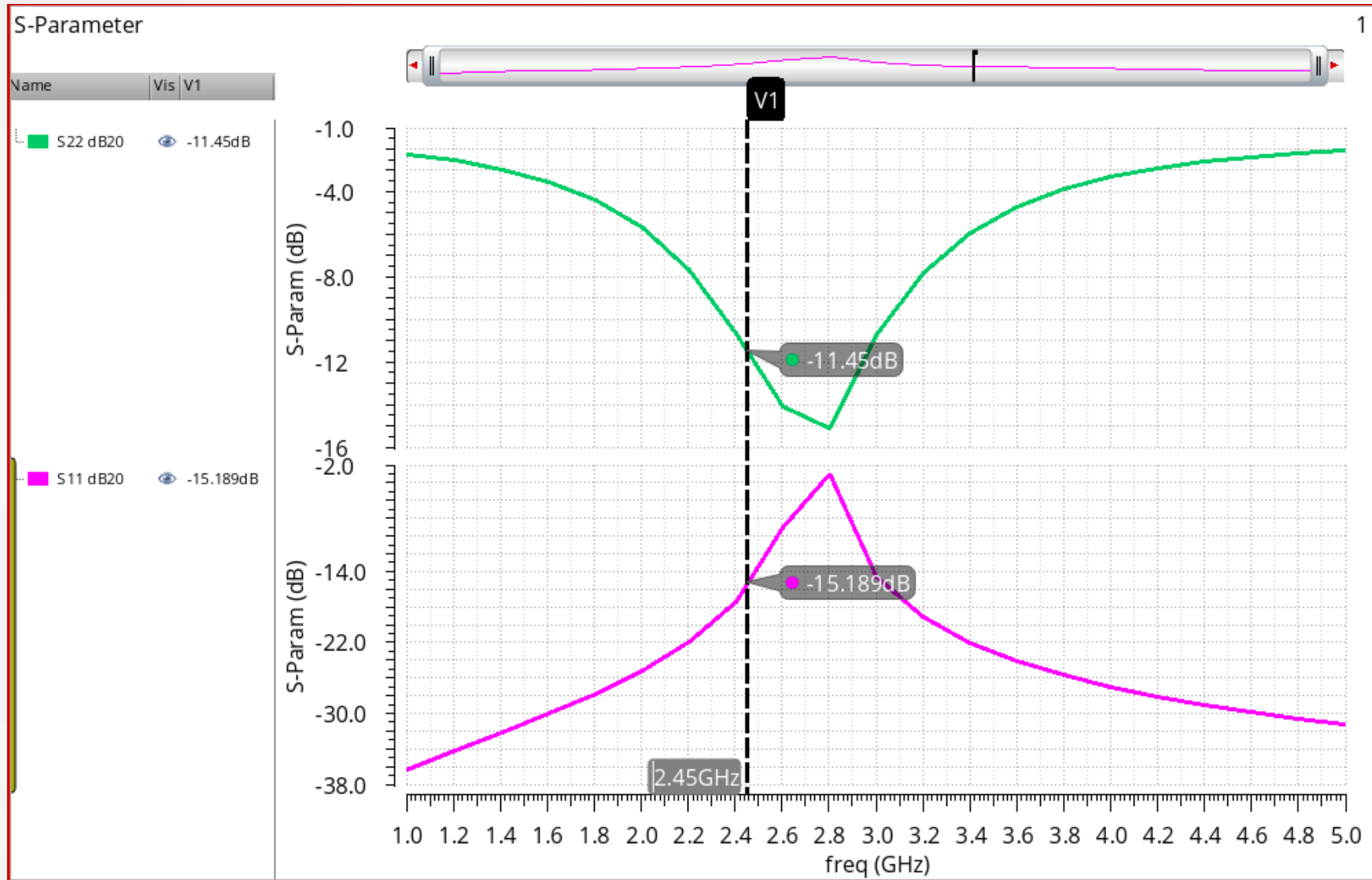


Receiver Design

Before Impedance Matching

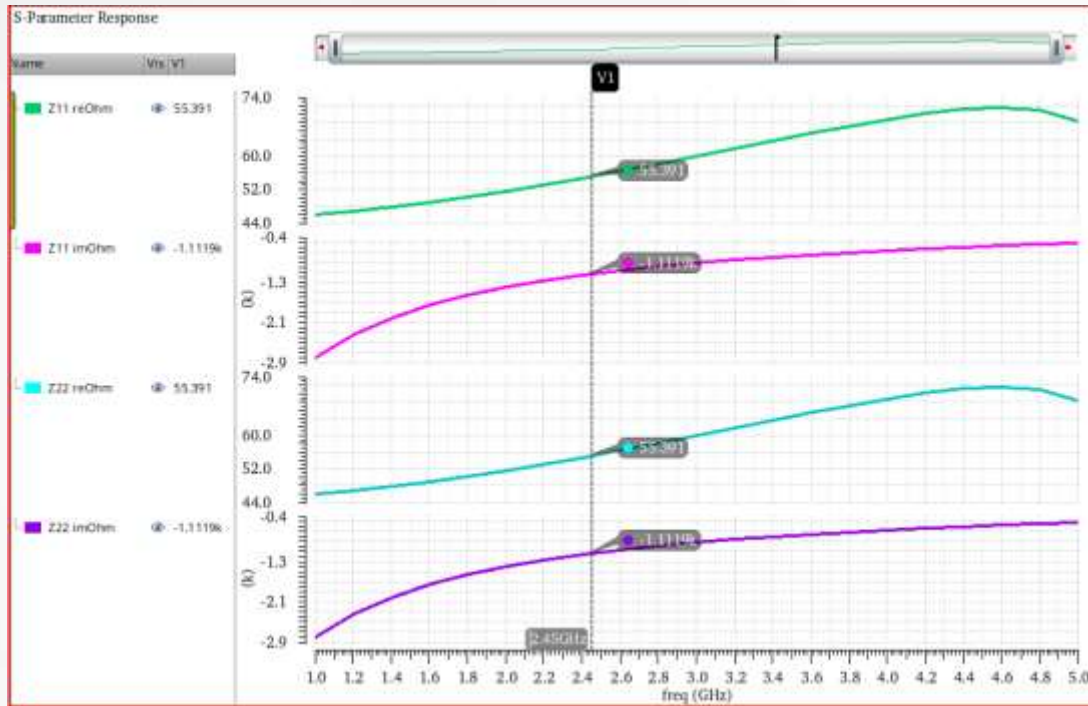


After Impedance Matching

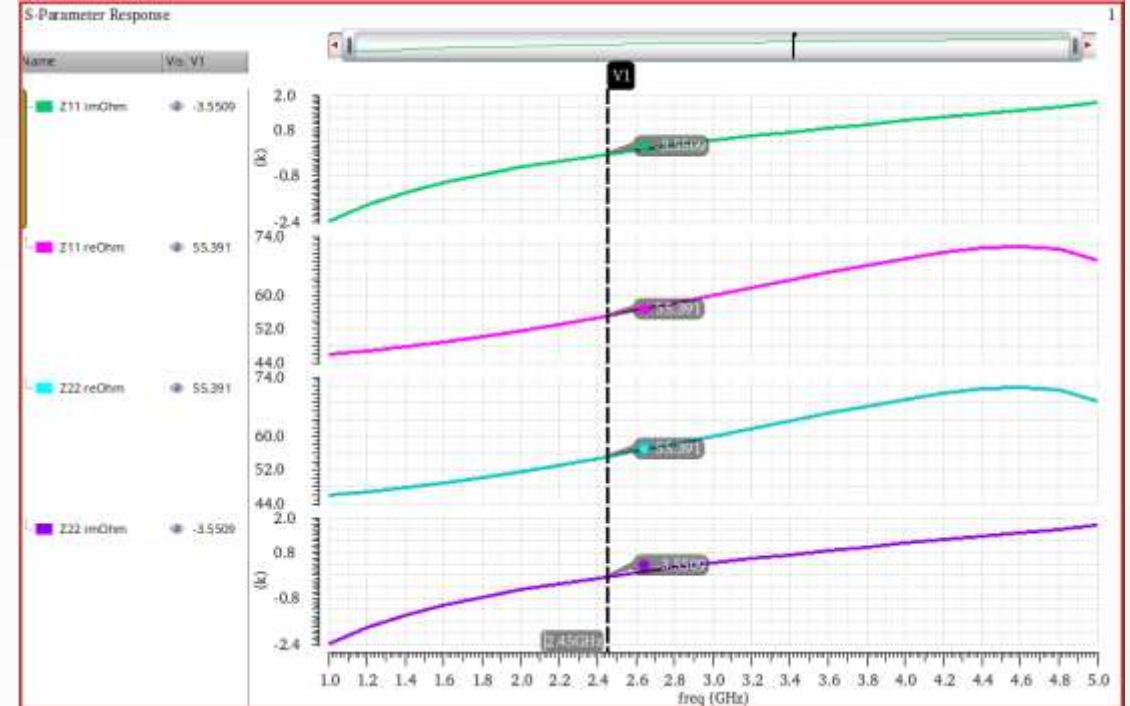


LNA Design

Differential LNA

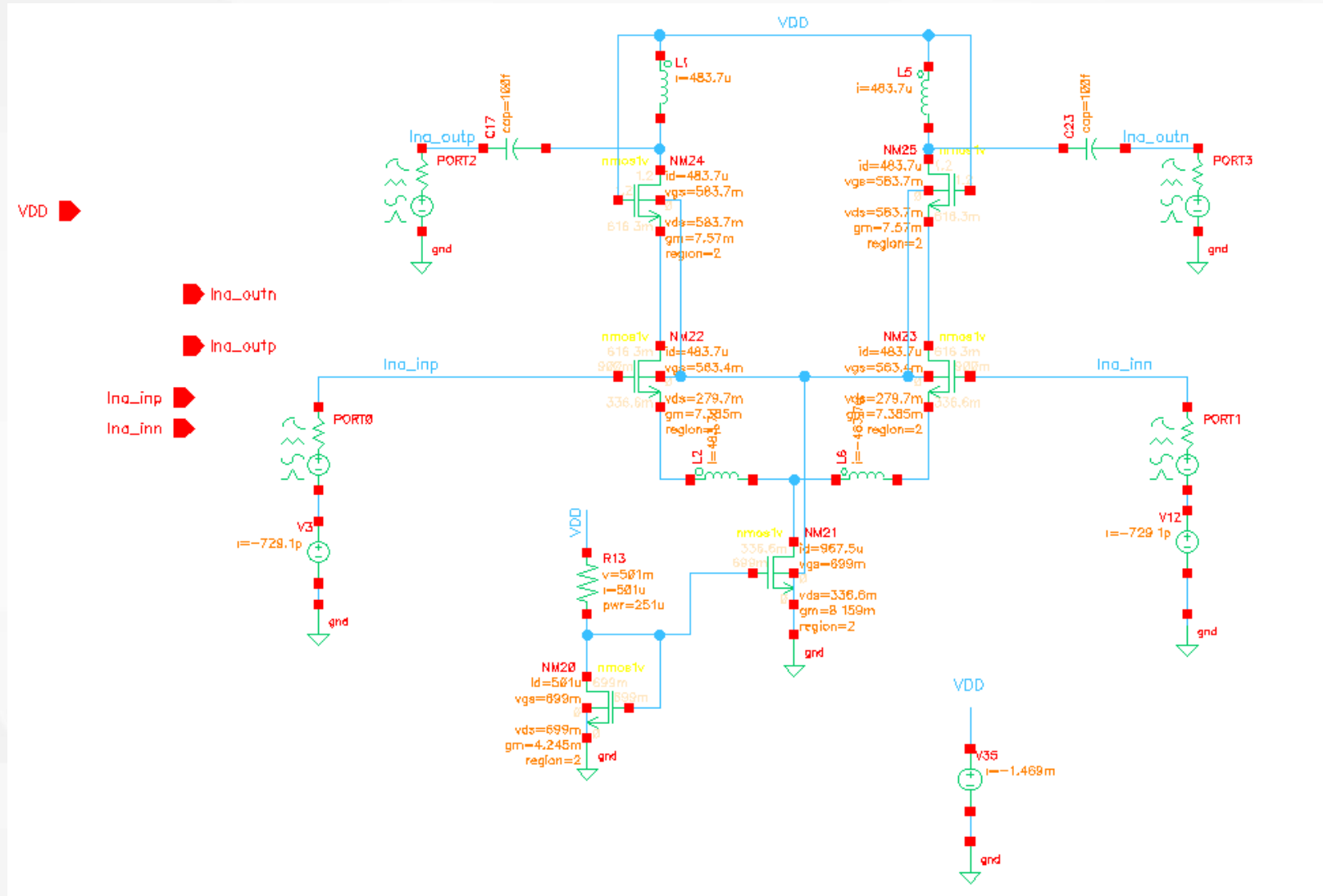


Receiver Design

Mixer + LPF (Noisy Output)

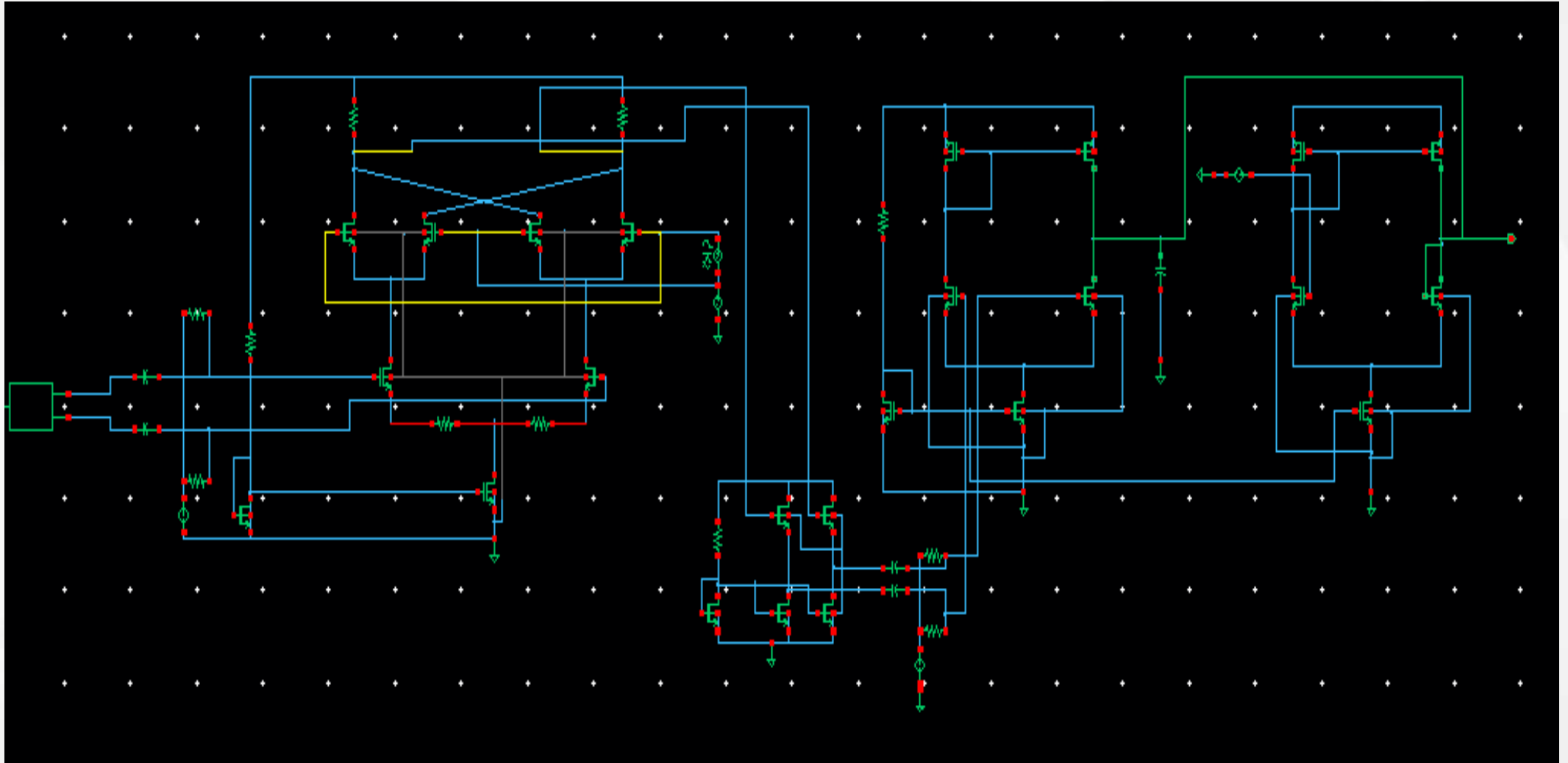


Receiver Design

Transient (Noisy)

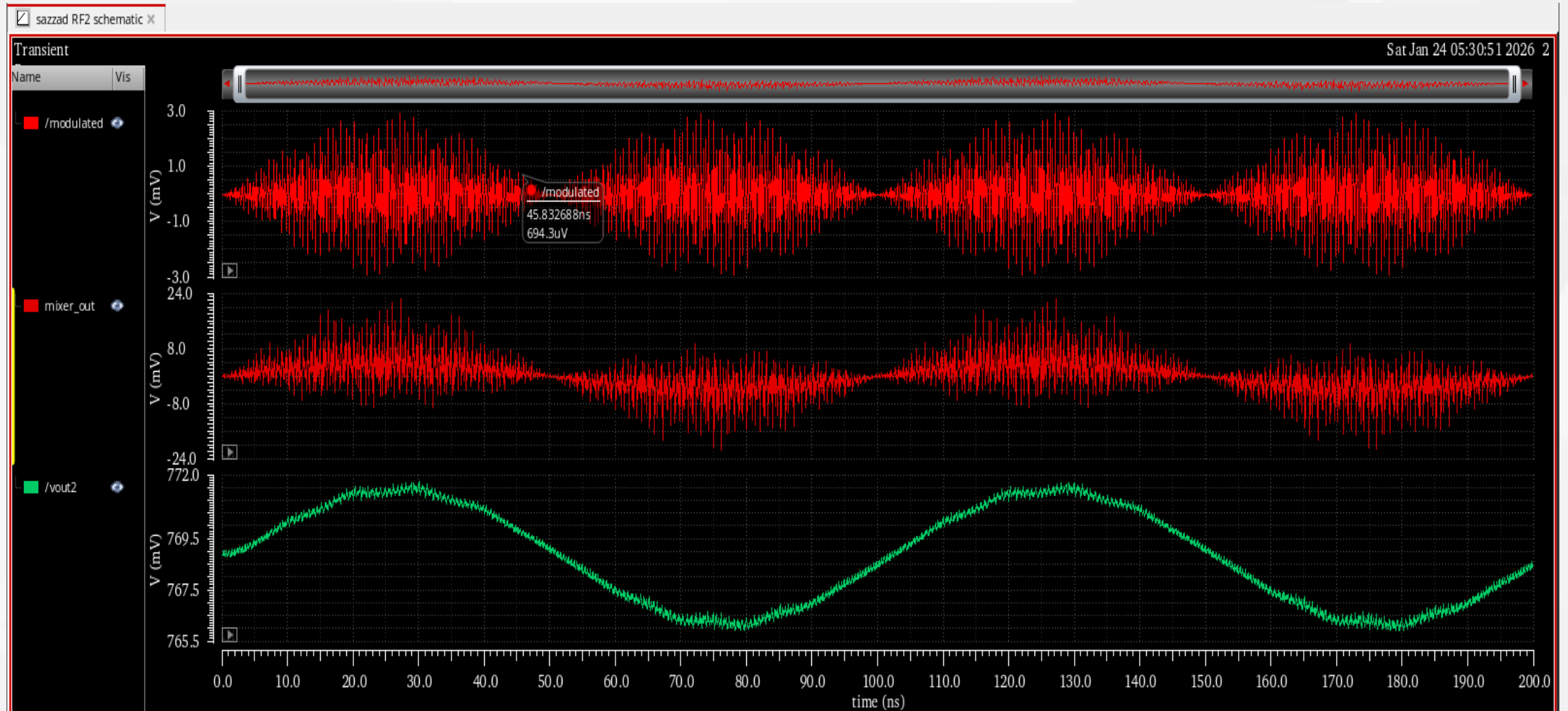


Receiver Design

LNA + Mixer + LPF (Clean Output)

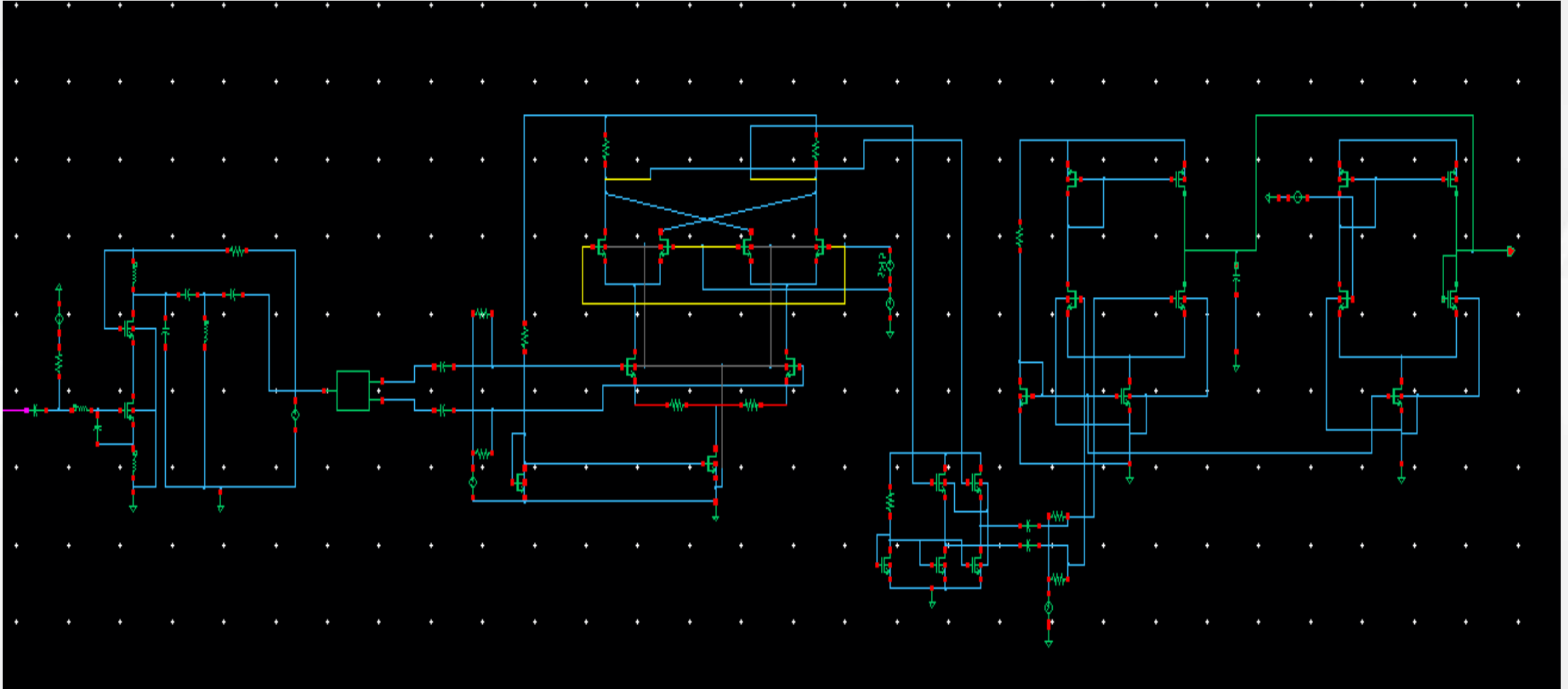

Receiver Design

Transient (Clean Output)

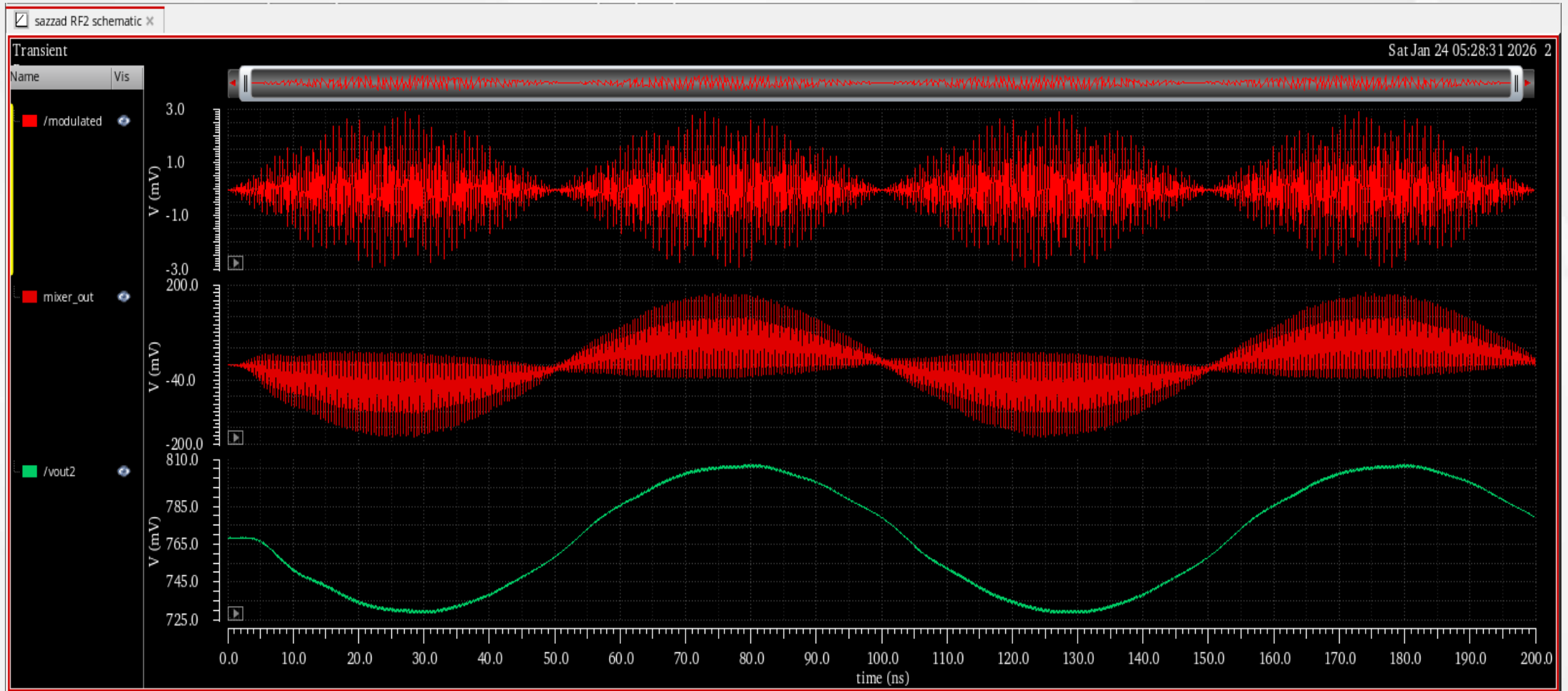

Receiver Design

NORMAL AM, DSB-SC, AND SSB SIGNALS:

